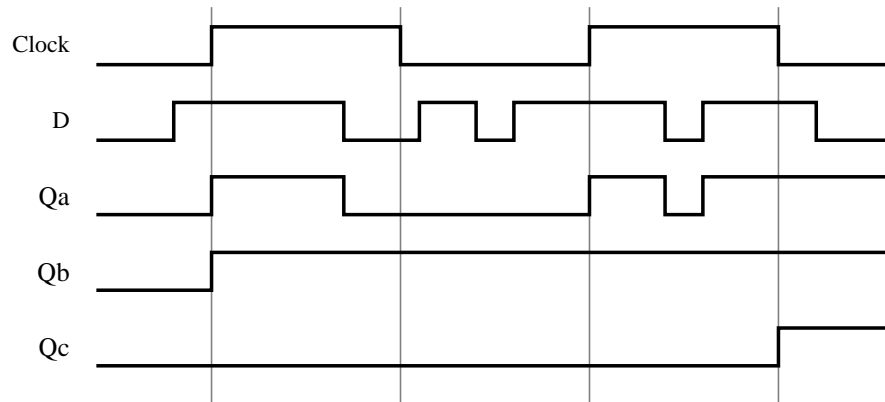



Chapter 7

7.1.




7.2. The circuit in Figure 7.3 can be modified to implement an SR latch by connecting S to the *Data* input and $S + R$ to the *Load* input. Thus the value of S is loaded into the latch whenever either S or R is asserted. Care must be taken to ensure that the *Data* signal remains stable while the *Load* signal is asserted.


7.3.

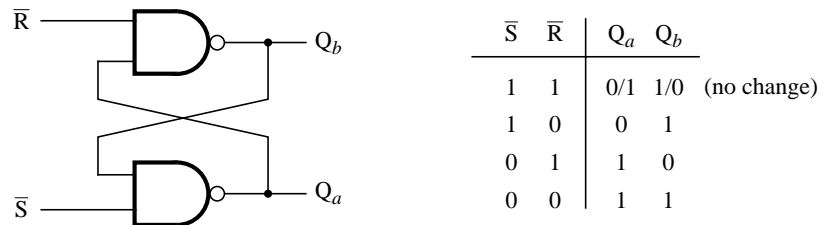


7.4.

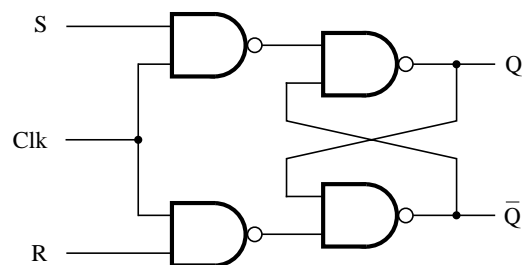


7.5.

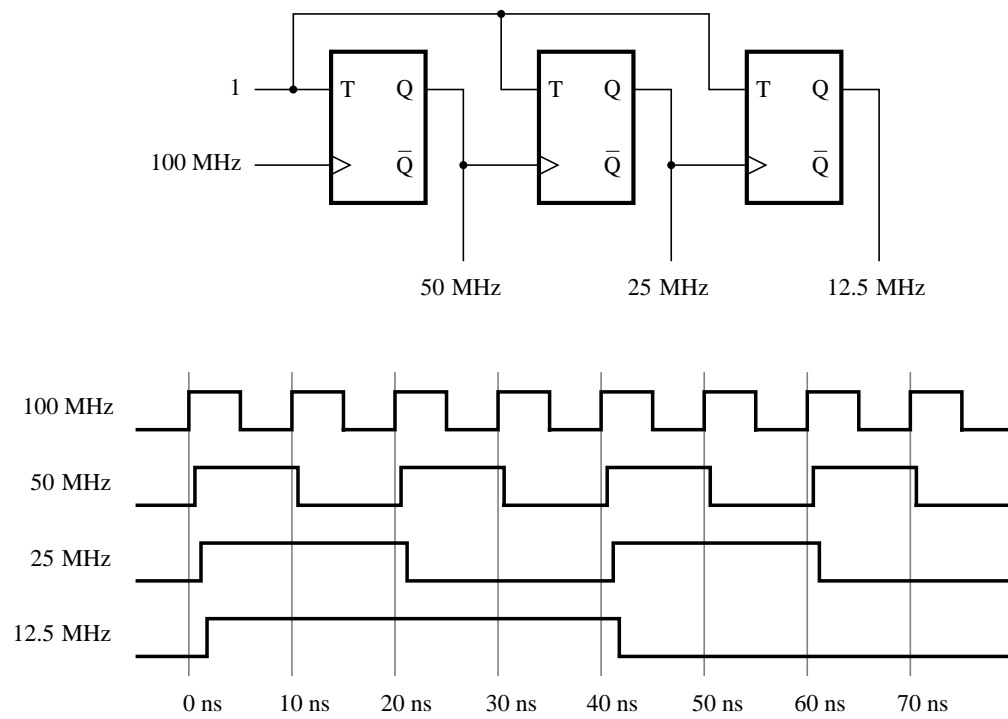


7.6.

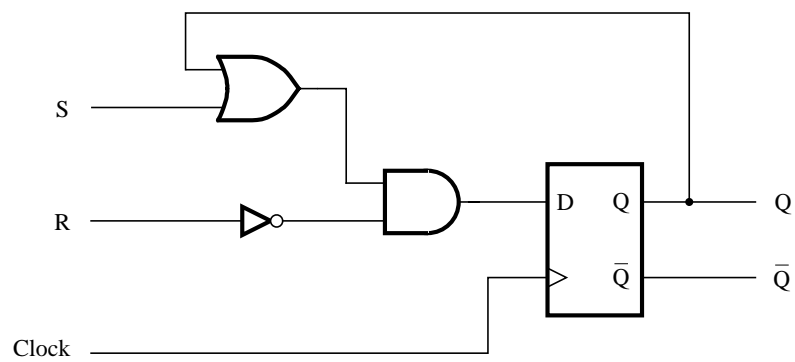


S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	0

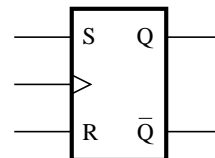


7.7.

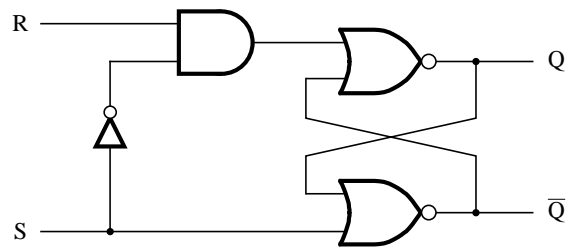

7.8.

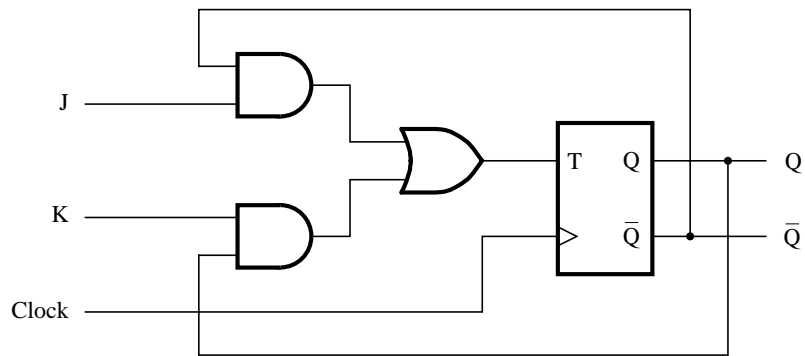

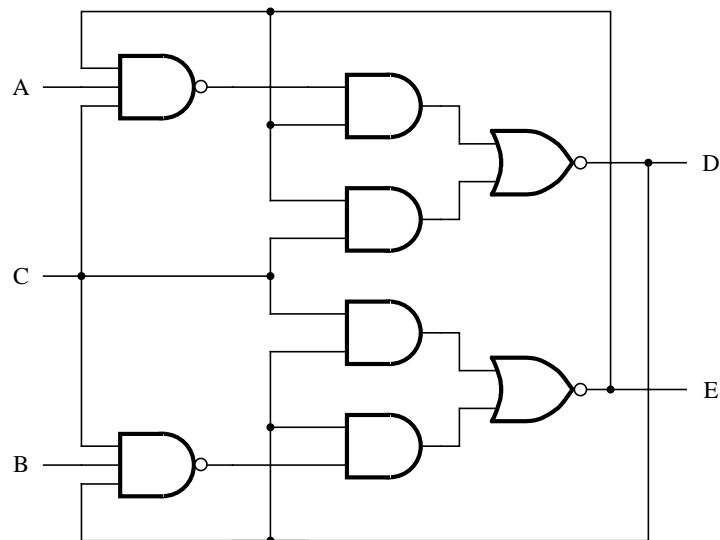7.9. As the circuit in Figure P7.2 is drawn, it is not a useful flip-flop circuit, because setting $C = 0$ results in both of the circuit outputs being set to 0. Consider the slightly modified circuit shown below:



This modified circuit acts as a negative-edge-triggered JK flip-flop, in which $J = A$, $K = B$, $Clock = C$, $Q = D$, and $\bar{Q} = E$. This circuit is found in the standard chip called 74LS107A (plus a *Clear* input, which is not shown).

```
7.10.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;
```

```
ENTITY prob7_10 IS
    PORT ( T, Resetn, Clock : IN  STD_LOGIC ;
           Q                  : OUT STD_LOGIC ) ;
END prob7_10 ;
```

```
ARCHITECTURE Behavior OF prob7_10 IS
    SIGNAL Qint : STD_LOGIC ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Qint <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            IF T = '1' THEN
                Qint <= NOT Qint ;
            ELSE
                Qint <= Qint ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Qint ;
END Behavior ;
```

```
7.11.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;
```

```
ENTITY prob7_11 IS
    PORT ( J, K, Resetn, Clock : IN  STD_LOGIC ;
           Q                  : OUT STD_LOGIC ) ;
END prob7_11 ;
```

```
ARCHITECTURE Behavior OF prob7_11 IS
    SIGNAL Qint : STD_LOGIC ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Qint <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Qint <= ( J AND NOT Qint ) OR ( NOT K AND Qint ) ;
        END IF ;
    END PROCESS ;
    Q <= Qint ;
END Behavior ;
```

- 7.13. Let $S = s_1s_0$ be a binary number that specifies the number of bit-positions to shift by. Also let L be a parallel-load input, and let $R = r_3r_2r_1r_0$ be parallel data. If the inputs to the flip-flops are $D_0 \dots D_3$ and the outputs are $Q_0 \dots Q_3$, then the barrel-shifter can be represented by the logic expressions

$$\begin{aligned} D_3 &= L \cdot R_3 + \overline{L} \cdot (\overline{s_1}\overline{s_0}q_3) \\ D_2 &= L \cdot R_2 + \overline{L} \cdot (\overline{s_1}\overline{s_0}q_2 + \overline{s_1}s_0q_3) \\ D_1 &= L \cdot R_1 + \overline{L} \cdot (\overline{s_1}\overline{s_0}q_1 + \overline{s_1}s_0q_2 + s_1\overline{s_0}q_3) \\ D_0 &= L \cdot R_0 + \overline{L} \cdot (\overline{s_1}\overline{s_0}q_0 + \overline{s_1}s_0q_1 + s_1\overline{s_0}q_2 + s_1s_0q_3) \end{aligned}$$

7.14.

```


LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY prob7_14 IS
    PORT ( R          : IN          STD_LOGIC_VECTOR (3 DOWNTO 0) ;
          Shift       : IN          STD_LOGIC_VECTOR (1 DOWNTO 0) ;
          L, Clock    : IN          STD_LOGIC ;
          Q           : BUFFER STD_LOGIC_VECTOR (3 DOWNTO 0) ) ;
END prob7_14 ;


ARCHITECTURE Behavior OF prob7_14 IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF L = '1' THEN
            Q <= R ;
        ELSE
            CASE Shift IS
                WHEN "10"    => Q <= "00" & Q(3 DOWNTO 2) ;
                WHEN "01"    => Q <= "0" & Q(3 DOWNTO 1) ;
                WHEN OTHERS => Q <= Q ;
            END CASE ;
        END IF ;
    END PROCESS ;
END Behavior ;

```


7.15.

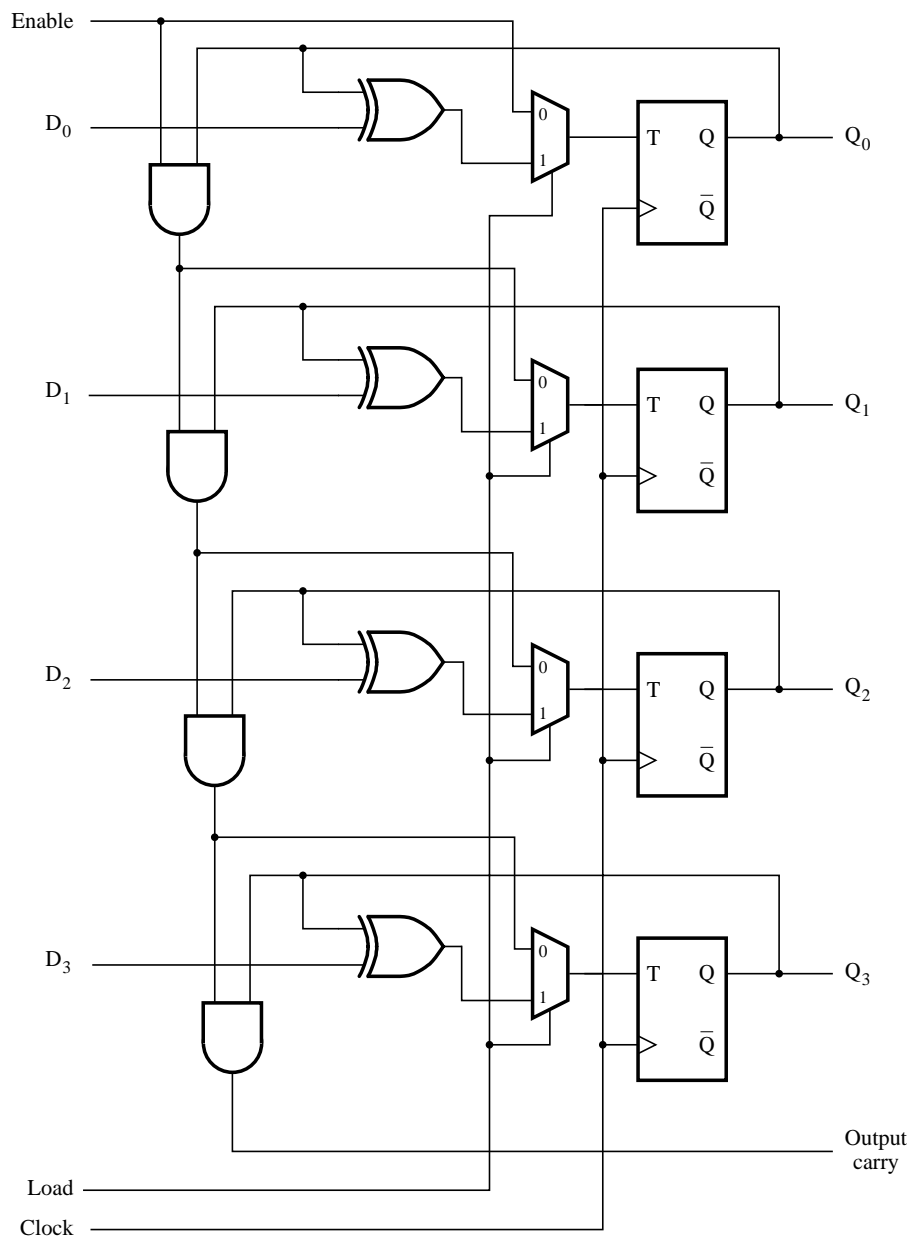

7.16.

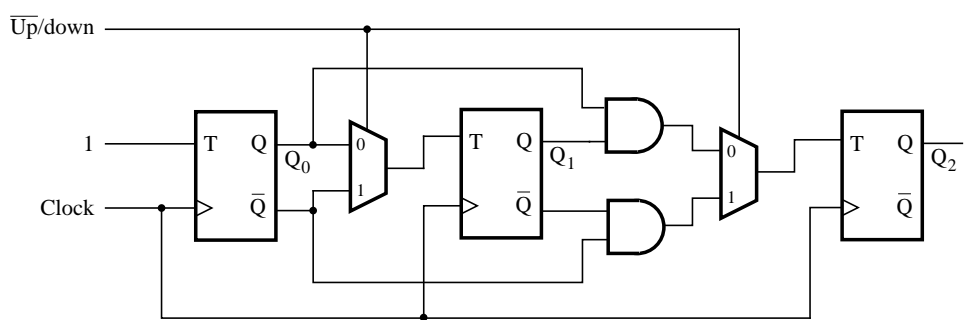


7.17.

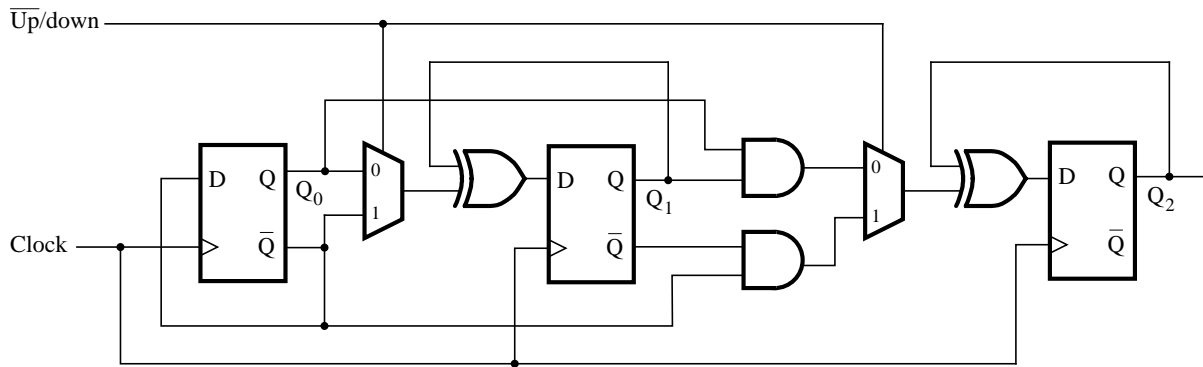

7.18. The counting sequence is 000, 001, 010, 111.

7.19. The circuit in Figure P7.4 is a master-slave JK flip-flop. It suffers from a problem sometimes called *ones-catching*. Consider the situation where the Q output is low, $Clock = 0$, and $J = K = 0$. Now let $Clock$ remain stable at 0 while J change from 0 to 1 and then back to 0. The master stage is now set to 1 and this value will be incorrectly transferred into the slave stage when the clock changes to 1.

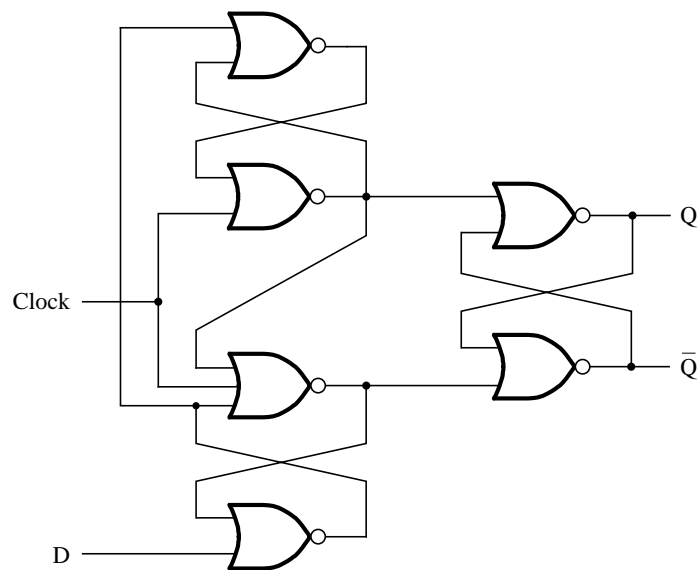7.20. Repeated application of DeMorgan's theorem can be used to change the positive-edge triggered D flip-flop in Figure 7.11 into the negative-edge D triggered flip-flop:



```

7.21.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;
        USE ieee.std_logic_unsigned.all ;

        ENTITY prob7_21 IS
            PORT ( R                : IN      STD_LOGIC_VECTOR(23 DOWNTO 0) ;
                  Clock, Resetn, L, U : IN      STD_LOGIC ;
                  Q                  : BUFFER STD_LOGIC_VECTOR(23 DOWNTO 0) ) ;
        END prob7_21 ;

```

```

        ARCHITECTURE Behavior OF prob7_21 IS
        BEGIN
            PROCESS ( Clock, Resetn )
            BEGIN
                IF Resetn = '0' THEN
                    Q <= (OTHERS => '0') ;
                ELSIF Clock'EVENT AND Clock = '1' THEN
                    IF L = '1' THEN
                        Q <= R ;
                    ELSIF U = '1' THEN
                        Q <= Q+1 ;
                    ELSE
                        Q <= Q-1 ;
                    END IF ;
                END IF ;
            END PROCESS ;
        END Behavior ;

```

```

7.22.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;
        USE ieee.std_logic_unsigned.all ;

        ENTITY prob7_22 IS
            GENERIC ( N : INTEGER := 4 ) ;
            PORT ( Clock, Resetn, E : IN      STD_LOGIC ;
                  Q                  : OUT STD_LOGIC_VECTOR ( N-1 DOWNTO 0) ) ;
        END prob7_22 ;

```

```

        ARCHITECTURE Behavior OF prob7_22 IS
            SIGNAL Count : STD_LOGIC_VECTOR ( N-1 DOWNTO 0 ) ;
        BEGIN
            PROCESS ( Clock, Resetn )
            BEGIN
                IF Resetn = '0' THEN
                    Count <= (OTHERS => '0') ;

                ... con't

```



```

        ELSIF Clock'EVENT AND Clock = '1' THEN
            IF E = '1' THEN
                Count <= Count + 1 ;
            ELSE
                Count <= Count ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;

```

7.23. LIBRARY ieee ;
 USE ieee.std_logic_1164.all ;

```

ENTITY prob7_23 IS
    PORT ( R           : IN      INTEGER RANGE 0 TO 11 ;
           Clock, Resetn, L : IN      STD_LOGIC ;
           Q             : BUFFER INTEGER RANGE 0 TO 11 ) ;
END prob7_23 ;

```

```

ARCHITECTURE Behavior OF prob7_23 IS
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Q <= 0 ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            IF L = '1' THEN
                Q <= R ;
            ELSE
                IF Q = 11 THEN
                    Q <= 0 ;
                ELSE
                    Q <= Q + 1 ;
                END IF ;
            END IF ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

7.24. The longest delay in the circuit is the from the output of FF₀ to the input of FF₃. This delay totals 5 ns. Thus the minimum period for which the circuit will operate reliably is

$$T_{min} = 5 \text{ ns} + t_{su} = 8 \text{ ns}$$

The maximum frequency is

$$F_{max} = 1/T_{min} = 125 \text{ MHz}$$

```

7.25.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY prob7_25 IS
            PORT ( Clock, Clear : IN          STD_LOGIC ;
                  BCD0, BCD1 : BUFFER STD_LOGIC_VECTOR(3 DOWNT0 0) ) ;
        END prob7_25 ;

        ARCHITECTURE Structure OF prob7_25 IS
            COMPONENT fig7_25
                PORT ( D                : IN          STD_LOGIC_VECTOR(3 DOWNT0 0) ;
                      Clock, Enable, Load : IN          STD_LOGIC ;
                      Q                  : BUFFER STD_LOGIC_VECTOR(3 DOWNT0 0) ) ;
            END COMPONENT ;
            SIGNAL Load0, Load1 : STD_LOGIC ;
            SIGNAL Enab0, Enab1 : STD_LOGIC ;
            SIGNAL Zero          : STD_LOGIC_VECTOR(3 DOWNT0 0) ;
        BEGIN
            Zero <= "0000" ;
            Enab0 <= '1' ;
            Enab1 <= BCD0(0) AND BCD0(3) ;

            Load0 <= Enab1 OR Clear ;
            Load1 <= (BCD1(0) AND BCD1(3)) OR Clear ;

            cnt0: fig7_25 PORT MAP ( Clock => Clock, Load => Load0, Enable => Enab0,
                                   D => Zero, Q => BCD0 ) ;
            cnt1: fig7_25 PORT MAP ( Clock => Clock, Load => Load1, Enable => Enab1,
                                   D => Zero, Q => BCD1 ) ;
        END Structure ;

```

```

7.26.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY prob7_26 IS
            PORT ( Clock, Resetn : IN          STD_LOGIC ;
                  Q               : BUFFER STD_LOGIC_VECTOR(0 TO 7) ) ;
        END prob7_26 ;

        ARCHITECTURE Behavior OF prob7_26 IS
        BEGIN
            PROCESS ( Clock, Resetn )
            BEGIN
                IF Resetn = '0' THEN
                    Q <= "00000000" ;
                ELSIF Clock'EVENT AND Clock = '1' THEN
                    Q <= (NOT Q(7)) & Q(0 TO 6) ;
                END IF ;
            END PROCESS ;
        END Behavior ;

```

```

7.27.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;

        ENTITY prob7_27 IS
            GENERIC ( N : INTEGER := 8 ) ;
            PORT ( Clock, Start : IN          STD_LOGIC ;
                  Q             : BUFFER STD_LOGIC_VECTOR(0 TO N-1) ) ;
        END prob7_27 ;

        ARCHITECTURE Behavior OF prob7_27 IS
        BEGIN
            PROCESS ( Clock, Start )
            BEGIN
                IF Start = '1' THEN
                    Q <= (OTHERS => '0') ;
                    Q(0) <= '1' ;
                ELSIF Clock'EVENT AND Clock = '1' THEN
                    GenBits: FOR i IN 1 TO N-1 LOOP
                        Q(i) <= Q(i-1) ;
                    END LOOP ;
                    Q(0) <= Q(N-1) ;
                END IF ;
            END PROCESS ;
        END Behavior ;

7.28.  LIBRARY ieee ;
        USE ieee.std_logic_1164.all ;
        USE ieee.std_logic_unsigned.all ;

        ENTITY prob7_28 IS
            PORT ( Clock, Reset : IN          STD_LOGIC ;
                  Data          : IN          STD_LOGIC_VECTOR(3 DOWNTO 0) ;
                  Q             : BUFFER STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
        END prob7_28 ;

        ARCHITECTURE Behavior OF prob7_28 IS
        BEGIN
            PROCESS ( Clock, Reset )
            BEGIN
                IF Reset = '1' THEN
                    Q <= "0000" ;
                ELSIF Clock'EVENT AND Clock = '1' THEN
                    Q <= Q + Data ;
                END IF ;
            END PROCESS ;
        END Behavior ;

```

7.29.

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
LIBRARY lpm ;
USE lpm.lpm_components.all ;

ENTITY prob7_29 IS
    PORT ( Clock, Reset : IN      STD_LOGIC ;
          Q              : OUT    STD_LOGIC_VECTOR(31 DOWNTO 0) );
END prob7_29 ;

ARCHITECTURE Structural OF prob7_29 IS
BEGIN
    cnt: lpm_counter
        GENERIC MAP ( lpm_width => 32 )
        PORT MAP ( clock => Clock, aclr => Reset, q => Q ) ;
END Structural ;

```

7.33.

	T_1	T_2	T_3
(Swap): I_4	$R_{out} = X, T_{in}$	$R_{out} = Y, R_{in} = X$	$T_{out}, R_{in} = Y,$ <i>Done</i>

Since the processor now has five operations a 3-to-8 decoder is needed to decode the signals f_2, f_1, f_0 . The SWAP operation is represented by the code

$$I_4 = f_2 \bar{f}_1 \bar{f}_0$$


New expressions are needed for R_{in} and R_{out} to accommodate the SWAP operation:

$$\begin{aligned}
 Rk_{in} &= (I_0 + I_1) \cdot T_1 \cdot X_k + (I_2 + I_3) \cdot T_3 \cdot X_k + I_4 \cdot T_2 \cdot X_k + I_4 \cdot T_3 \cdot Y_k \\
 Rk_{out} &= I_1 \cdot T_1 \cdot Y_k + (I_2 + I_3) \cdot (T_1 X_k + T_2 Y_k) + I_4 \cdot T_1 X_k + I_4 \cdot T_2 Y_k
 \end{aligned}$$

The control signals for the temporary register, T , are

$$\begin{aligned}
 T_{in} &= T_1 I_4 \\
 T_{out} &= T_3 I_4
 \end{aligned}$$


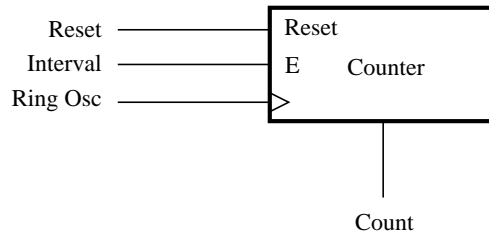
7.34. (a) Period = $2 \times n \times t_p$
(b)



The counter tallies the number of pulses in the 100 ns time period. Thus

$$t_p = \frac{100 \text{ ns}}{2 \times \text{Count} \times n}$$

7.35.

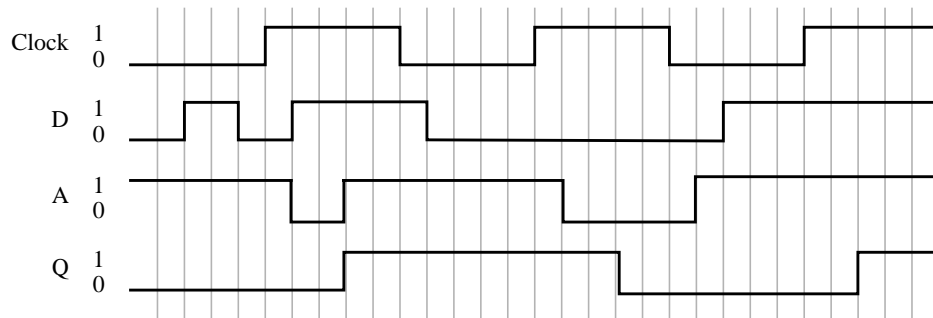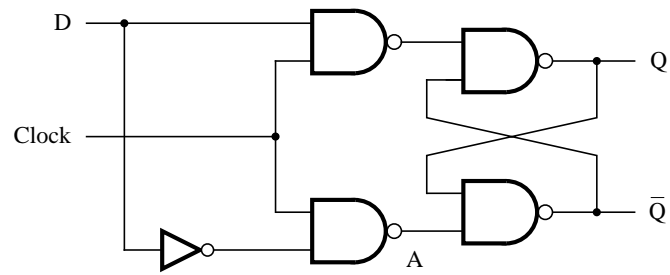

7.36.

