


Circuitos Lógicos e Organização de Computadores

Capítulo 8 –Circuitos Sequenciais Síncronos

Ricardo Pannain

pannain@unicamp.br

 Forma geral de um circuito sequencial - MOORE



Máquina de estados finitos (FSM – Finite State Machine) → o comportamento do circuito pode ser representado usando um número finito de estados.

Máquina de MOORE → saídas dependem apenas do estado do circuito.

Etapas Básicas de Projeto

Exemplo:

Supondo um circuito que tenha uma entrada w e uma saída z .

- Todas as mudanças ocorrerão na subida do clock.
- A saída z é igual a 1 se durante dois ciclos consecutivos imediatamente precedente a entrada w for igual a 1. Caso contrário o valor é zero.

A tabela abaixo ilustra o funcionamento para um padrão de w qualquer.

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Etapas Básicas de Projeto

PRIMEIRO PASSO → Diagrama de estados

Determinar quantos estados são necessários e quais transições são possíveis de um estado para outro.

No exemplo:

Supondo o estado inicial A (com saída $z = 0$) → enquanto $w = 0$ ele permanece neste estado.

Se $w = 1$, na subida do clock ele passará para o estado B (com $z = 0$).

Uma vez no estado B, se $w = 0$, ele passará para o estado A ($z = 0$) na subida do clock.

Se $w = 1$, passará para um terceiro estado C ($z = 1$).

No estado C, se $w = 0$, ele passará para o estado A ($z = 0$) na subida do clock. Se $w = 1$, Continuará no estado C ($z = 1$)

Diagrama de estados do exemplo anterior – Máquina de MOORE


 



Diagrama de estados do exemplo anterior – Máquina de MOORE

 

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Tabela de estados


SEGUNDO PASSO → Tabela de Estados

 

Present state	Next state		Output z
	$w = 0$	$w = 1$	

Tabela de estados

SEGUNDO PASSO → Tabela de Estados

 

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Circuito seqüencial geral

Como temos 3 estados, precisaremos de 2 Flip-Flops e o circuito ficaria:

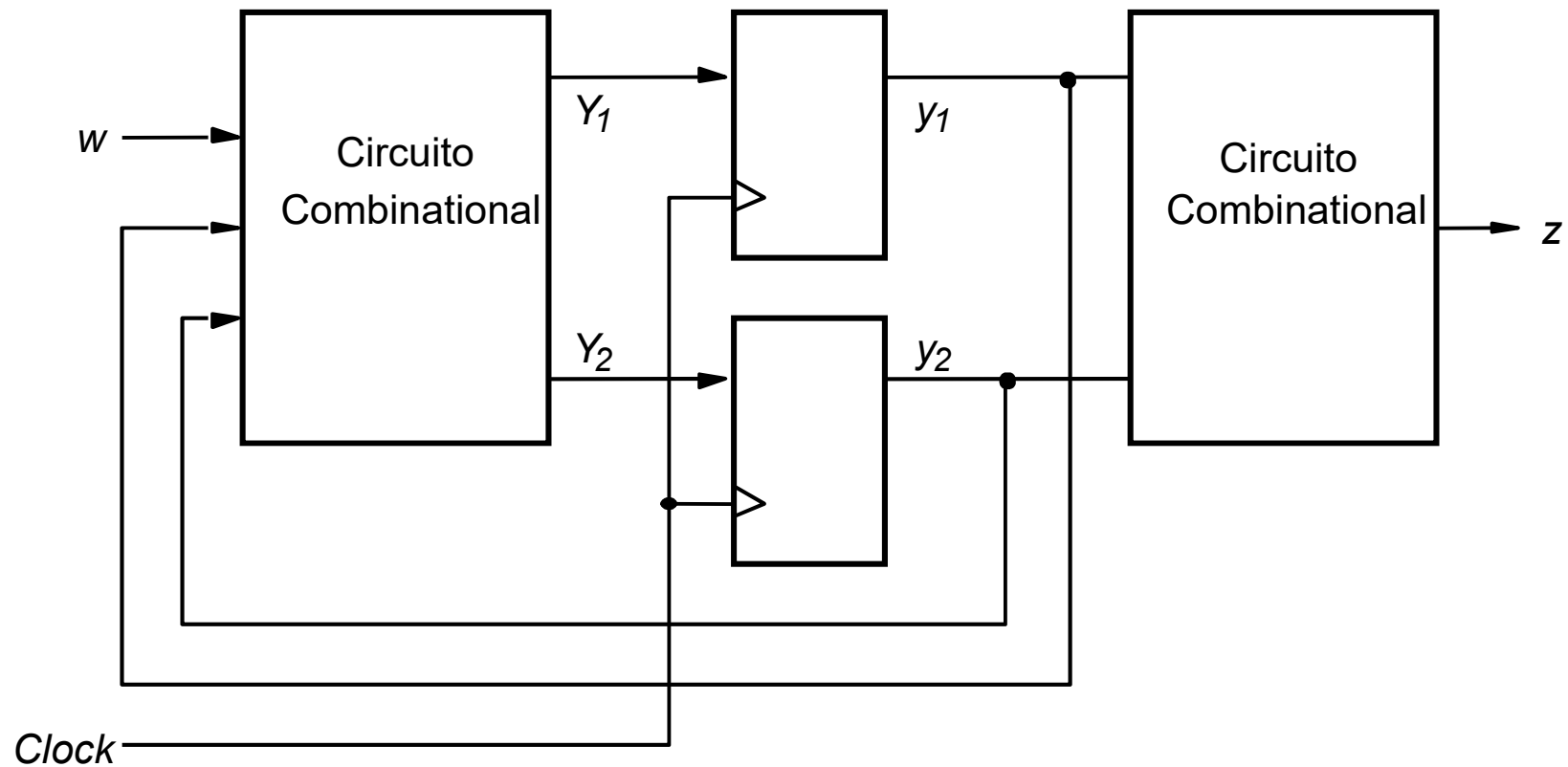


Tabela de estados

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Tabela de estados assinalados

	Present state	Next state		Output z
		$w = 0$	$w = 1$	
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

Tabela de estados assinalados

	Present state y_2y_1	Next state		Output z
		$w = 0$	$w = 1$	
		Y_2Y_1	Y_2Y_1	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

w	y2	y1	Y2	Y1
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	d	d
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	d	d

y2	y1	z
0	0	0
0	1	0
1	0	1
1	1	d

Tabelas Verdade

Derivando as expressões lógicas dos próximos estados e da saída

$y_2 y_1$		00	01	11	10
		0	0	d	0
w	0	0	0	d	0
	1	1	0	d	0

$y_2 y_1$		00	01	11	10
		0	0	d	0
w	0	0	0	d	0
	1	0	1	d	1

y_2		0	1
		0	0
y_1	0	0	0
	1	1	d

Ignorando don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

$$Y_2 = wy_1\bar{y}_2 + w\bar{y}_1y_2$$

$$z = \bar{y}_1y_2$$

Usando don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$

$$z = y_2$$

Circuito Seqüencial do exemplo anterior



 


Diagrama de tempo do exemplo anterior

 

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w:	0	1	0	1	1	0	1	1	1	0	1
z:	0	0	0	0	0	1	0	0	1	1	0

Sistema digital com k registradores

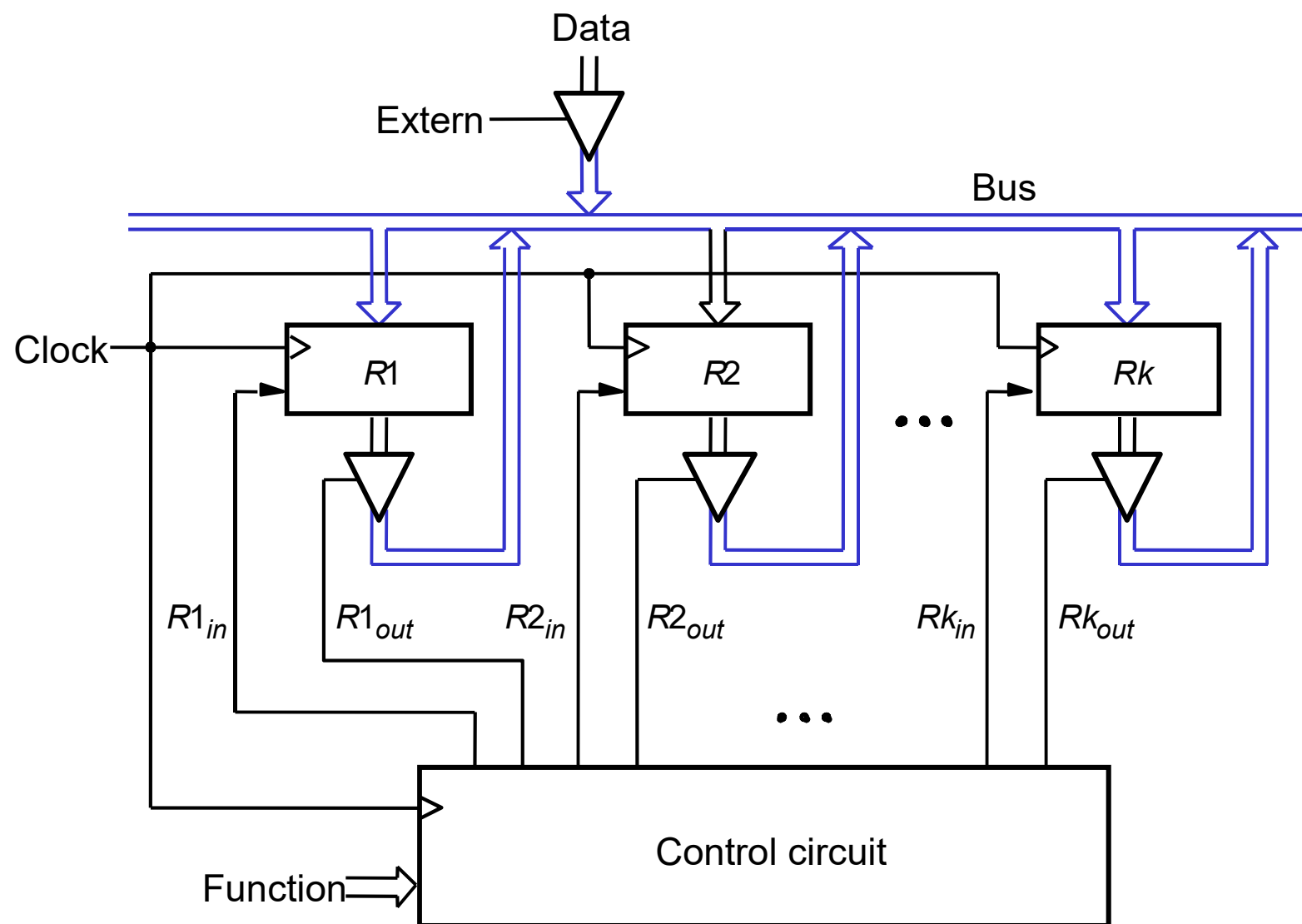

Exemplo – Troca de conteúdo entre dois registradores MOORE

Trocar o conteúdo dos registradores R1 e R2, utilizando o registrador R3 com auxiliar.
A troca se inicia quando $w=1$. A operação só termina quando a troca for feita, independente de w (gera done).

$R3 \leftarrow R2$

$R2 \leftarrow R1$

$R1 \leftarrow R3$

Sinais necessários

 


Diagrama de estados


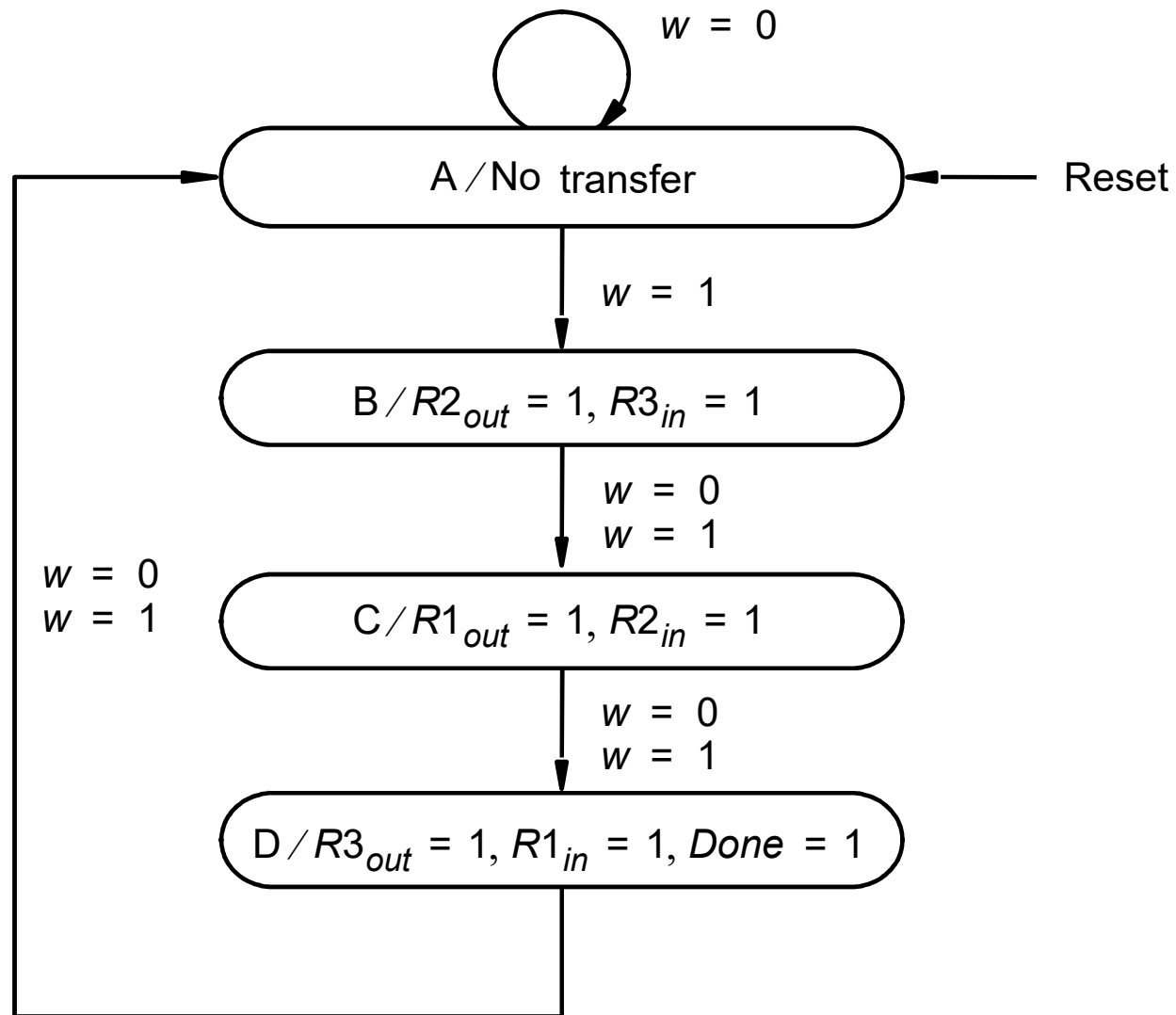


Diagrama de estados

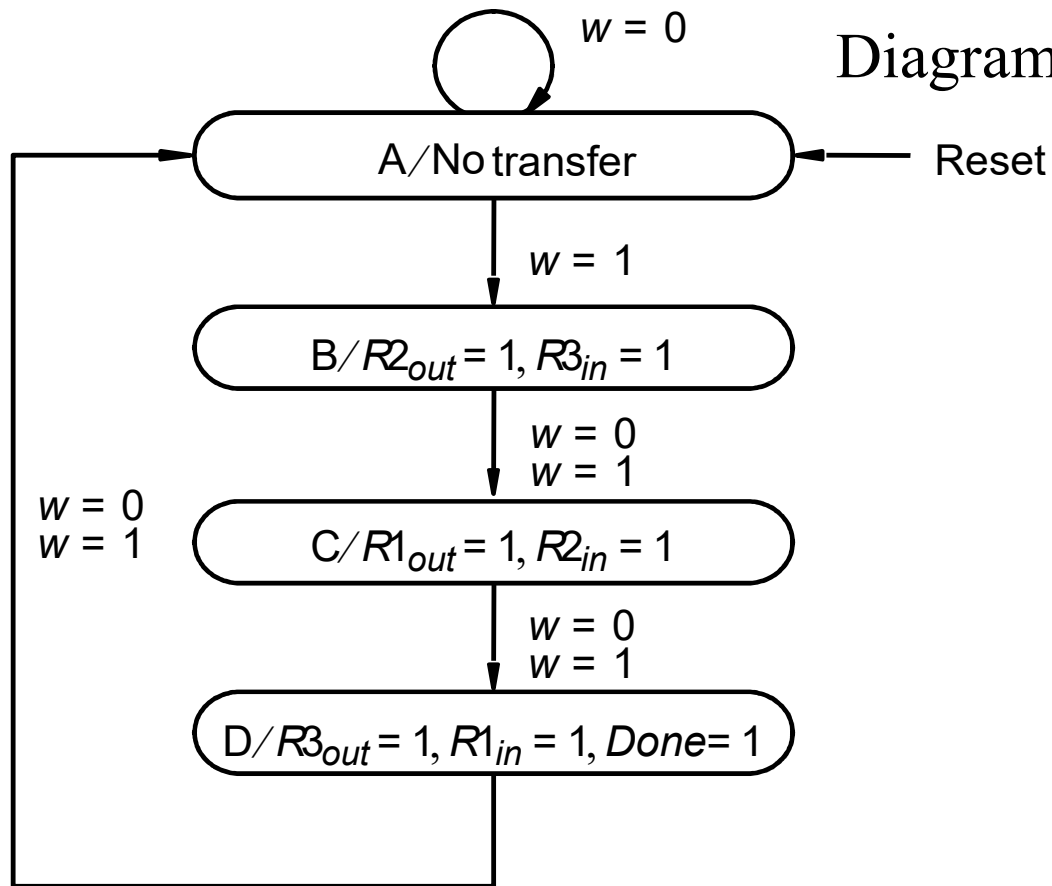

18

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	<i>Done</i>
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

Tabela de estados

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

Tabela de estados assinalados

	Present state y_2y_1	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1


Tabela de estados assinalados

	Present state y_2y_1	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1


w	y2	y1	Y2	Y1
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Derivação da expressão do próximo estado

w	y2	y1	Y2	Y1
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

 

$$Y_1 = w\bar{y}_1 + \bar{y}_1 y_2$$

 

$$Y_2 = y_1 \bar{y}_2 + \bar{y}_1 y_2$$

Tabela de estados assinalados

	Present state y_2y_1	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0 1	0	0	0	0	0	0	0
B	01	10	1 0	0	0	1	0	0	1	0
C	10	11	1 1	1	0	0	1	0	0	0
D	11	00	0 0	0	1	0	0	1	0	1

y2	y1	R1 out	R1 in	R2 out	R2 in	R3 out	R3 in	Done
0	0	0	0	0	0	0	0	0
0	1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0	0
1	1	0	1	0	0	1	0	1

Derivação das expressões das saídas

y2 y1	0	1
0	0	1
1	0	0

$$R2_{out}, R3_{in} = y'1y2$$


y2 y1	0	1
0	0	0
1	1	0

$$R1_{out}, R2_{in} = y1y'2$$

y2 y1	0	1
0	0	0
1	0	1

$$R3_{out}, R1_{in}, Done = y1y2$$

Circuito sequencial correspondente

 

Circuito seqüencial correspondente


$$R2_{out}, R3_{in} = y'1y2$$

$$R1_{out}, R2_{in} = y1y'2$$

$$R3_{out}, R1_{in}, Done = y1y2$$

$$Y1 = wy1' + y1'y2$$

$$Y2 = y1y2' + y1'y2$$

 

Problemas de assinalamento de estados

Suponha que, no primeiro exemplo, ao assinalar valores para os estados presentes, tenhamos escolhido conforma a tabela abaixo:

	Present state y_2y_1	Next state		Output z
		$w = 0$	$w = 1$	
		Y_2Y_1	Y_2Y_1	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	<i>dd</i>	<i>dd</i>	<i>d</i>

Problemas de assinalamento de estados

Suponha que, no primeiro exemplo, ao assinalar valores para os estados presentes, tenhamos escolhido conforma a tabela abaixo:

$$Y_1 = D_1 = w$$

$$Y_2 = D_2 = w y_1$$


$$z = y_2$$

w	y2	y1	Y2	Y1
0	0	0	0	0
0	0	1	0	0
0	1	0	d	d
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	0	d	d
1	1	1	1	1

	Present state $y_2 y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	dd	dd	d

Y2	00	01	11	10		Y2	00	01	11	10
0	0	0	0	d		0	0	0	0	d
1	0	1	1	d		1	1	1	1	d
	Y2 = wy1						Y1 = w			

Circuito com a melhoria no assinalamento

 

Circuito com a melhoria no assinalamento

 
 


Tabela de estados com melhoria de assnalamento – exemplo 2

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
	y_2y_1	Y_2Y_1	Y_2Y_1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	0 0	01	0	0	0	0	0	0	0
B	01	1 1	11	0	0	1	0	0	1	0
C	11	1 0	10	1	0	0	1	0	0	0
D	10	0 0	00	0	1	0	0	1	0	1

Derivação da expressão do próximo estado


$y_2 y_1$		w			
		00	01	11	10
0			1		
1		1	1		

$$Y_1 = w\bar{y}_2 + y_1\bar{y}_2$$

$y_2 y_1$		w			
		00	01	11	10
0			1	1	
1			1	1	

$$Y_2 = y_1$$

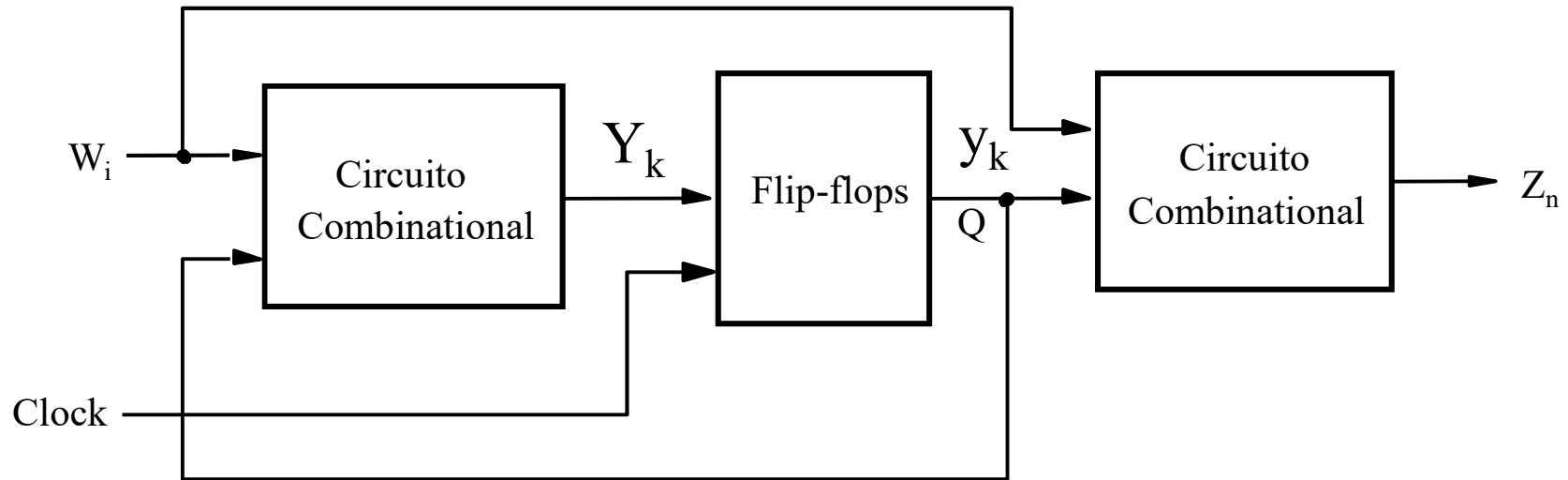Forma geral de um circuito sequencial - MEALY



Máquina de estados finitos (FSM – Finite State Machine) → o comportamento do circuito pode ser representado usando um número finito de estados.

Máquina de MEALY → saídas dependem do estado atual do circuito e das entradas.

Máquina de Mealy

Nos exemplos anteriores, os circuitos sequenciais onde cada estado tem valores dos sinais de saídas associados a eles, são chamadas **Máquinas de MOORE**.

Os circuitos sequenciais onde os sinais das saídas estão associados tanto aos estados como às entradas são chamadas de **Máquina de MEALY**

Tomando o primeiro exemplo visto anteriormente, que gerava $z = 1$ quando a ocorrência de $w = 1$ era detectada em dois períodos consecutivos de clock. Supondo agora que queiramos que z seja 1 no segundo ciclo que $w = 1$ seja detectado, como exemplifica a tabela abaixo:

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Diagrama de estado

No exemplo:

Supondo o estado inicial A \rightarrow enquanto $w = 0$ ele permanece neste estado e produz a saída $z = 0$. Se $w = 1$ ($z = 0$), na subida do clock, ele passará para o estado B. Uma vez no estado B, se $w = 0$ ($z = 0$), ele passará para o estado A na subida do clock. Se $w = 1$ produzirá a saída $z = 1$ e permanecerá neste estado..


 


Tabela de estados

 

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Tabela de estados assinalados

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1


w	y	Y
0	0	0
0	1	0
1	0	1
1	1	1

w	y	z
0	0	0
0	1	0
1	0	0
1	1	1


$$Y = wy' + wy = w$$

$$z = wy$$

Implementação da FSM

 


(a) Circuito

 

 
(b) Diagrama de tempo

Implementação da FSM incluindo um atraso na saída



OBS – Mesmo
circuito do slide 29

(a) Circuit

 

(b) Timing diagram

Exemplo – Troca de conteúdo entre dois registradores - Mealy


Trocar o conteúdo dos registradores R1 e R2, utilizando o registrador R3 com auxiliar

$R3 \leftarrow R2$


$R2 \leftarrow R1$


$R1 \leftarrow R3$

Sinais necessários

 


 Exemplo – troca de conteúdo de registradores



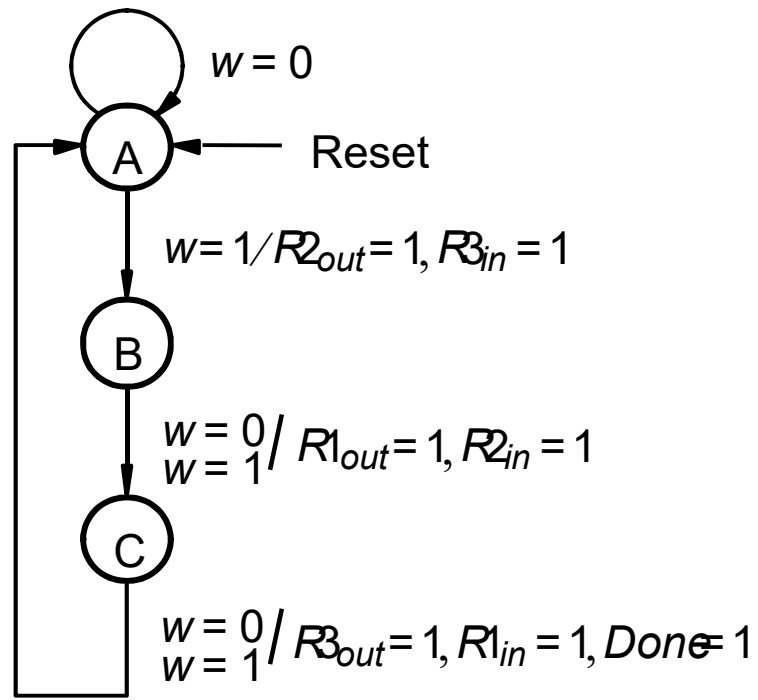

estado atual	Próximo Estado		saídas													
			R1out		R1in		R2out		R2in		R3out		R3in		done	
y2y1	Y2	Y1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1
	y2y1	y2y1														
A	A	B	0	0	0	0	0	1	0	0	0	0	0	1	0	0
B	C	C	1	1	0	0	0	0	1	1	0	0	0	0	0	0
C	A	A	0	0	1	1	0	0	0	0	1	1	0	0	1	1

 

estado atual	Próximo Estado		saídas													
y2y1	Y2	Y1	R1out		R1in		R2out		R2in		R3out		R3in		done	
	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1
	y2y1	y2y1														
A	00	A 00	B 01	0	0	0	0	1	0	0	0	0	0	1	0	0
B	01	C 10	C 10	1	1	0	0	0	1	1	0	0	0	0	0	0
C	10	A 00	A 00	0	0	1	1	0	0	0	1	1	0	0	1	1
	11	dd	dd	d	d	d	d	d	d	d	d	d	d	d	d	d

estado atual	Próximo Estado			saídas													
y2y1	Y2	Y1	R1out		R1in		R2out		R2in		R3out		R3in		done		
	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	w = 0	w = 1	
	y2y1	y2y1															
A	00	A 00	B 01	0	0	0	0	0	1	0	0	0	0	0	1	0	0
B	01	C 10	C 10	1	1	0	0	0	0	1	1	0	0	0	0	0	0
C	10	A 00	A 00	0	0	1	1	0	0	0	0	1	1	0	0	1	1
	11	dd	dd	d	d	d	d	d	d	d	d	d	d	d	d	d	d

$$Y2 = y1$$

y2y1	00	01	11	10
w				
0	0	1	d	0
1	0	1	d	0

$$Y1 = y2'y1'w$$

y2y1	00	01	11	10
w				
0	0	0	d	0
1	1	0	d	0

$$R2out, R3in = y2'y1'w$$

y2y1	00	01	11	10
w				
0	0	0	d	0
1	1	0	d	0

$$R1out, R2in = y1$$

y2y1	00	01	11	10
w				
0	0	1	d	0
1	0	1	d	0

$$R3out, R2in, done = y2$$

y2y1	00	01	11	10
w				
0	0	0	d	1
1	0	0	d	1

```

USE ieee.std_logic_1164.all ;

ENTITY simple IS
    PORT ( Clock, Resetn, w : IN  STD_LOGIC ;
          z : OUT STD_LOGIC ) ;
END simple ;

ARCHITECTURE Behavior OF simple IS
    TYPE State_type IS (A, B, C) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            con't ...
        
```


Figure 8.29a VHDL code for a simple FSM

```


CASE y IS
  WHEN A =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= B ;
    END IF ;
  WHEN B =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= C ;
    END IF ;
  WHEN C =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= C ;
    END IF ;
END CASE ;
END IF ;
END PROCESS ;
z <= '1' WHEN y = C ELSE '0' ;
END Behavior ;

```

Figure 8.29b VHDL code for a simple FSM (con't)

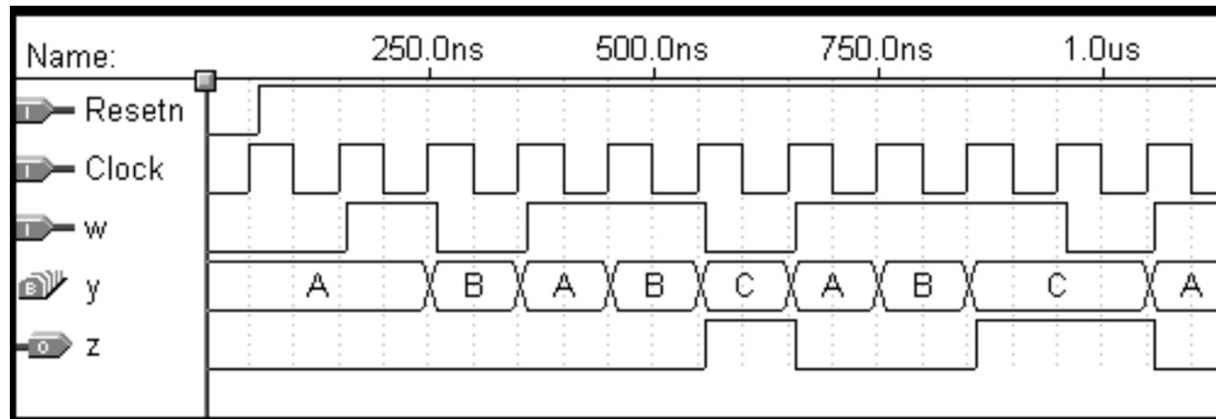

(a) Timing simulation results

 

(b) Magnified simulation results, showing timing details

Figure 8.32 Simulation results

(ENTITY declaration not shown)

ARCHITECTURE Behavior OF simple IS

 TYPE State_type IS (A, B, C) ;

 SIGNAL y_present, y_next : State_type ;

BEGIN

 PROCESS (w, y_present)

 BEGIN

 CASE y_present IS

 WHEN A =>

 IF w = '0' THEN

 y_next <= A ;

 ELSE

 y_next <= B ;

 END IF ;

 WHEN B =>

 IF w = '0' THEN

 y_next <= A ;

 ELSE

 y_next <= C ;

 END IF ;

Figure 8.33a Alternative style of code for an FSM


```

        WHEN C =>
            IF w = '0' THEN
                y_next <= A ;
            ELSE
                y_next <= C ;
            END IF ;
        END CASE ;
    END PROCESS ;

PROCESS (Clock, Resetn)
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;

z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;

```

Figure 8.33b Alternative style of code for an FSM (con't)


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY simple IS
    PORT (   Clock, Reseth, w      : IN  STD_LOGIC ;
            z                      : OUT  STD_LOGIC ) ;
END simple ;

ARCHITECTURE Behavior OF simple IS
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);
    CONSTANT A : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00" ;
    CONSTANT B : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01" ;
    CONSTANT C : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11" ;
BEGIN
    PROCESS ( w, y_present )
    BEGIN
        CASE y_present IS
            WHEN A =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= B ;
                END IF ;

... con't

```

Figure 8.35a Using constants for manual state assignment

```

        WHEN B =>
            IF w = '0' THEN y_next <= A ;
            ELSE y_next <= C ;
            END IF ;
        WHEN C =>
            IF w = '0' THEN y_next <= A ;
            ELSE y_next <= C ;
            END IF ;
        WHEN OTHERS =>
            y_next <= A ;
    END CASE ;
END PROCESS ;

PROCESS ( Clock, Resetn )
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;
z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;

```

Figure 8.35b Using constants for manual state assignment (cont')

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mealy IS
    PORT ( Clock, Resetn, w      : IN    STD_LOGIC ;
          z                      : OUT   STD_LOGIC ) ;
END mealy ;

ARCHITECTURE Behavior OF mealy IS
    TYPE State_type IS (A, B) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            CASE y IS
                WHEN A =>
                    IF w = '0' THEN y <= A ;
                    ELSE y <= B ;
                    END IF ;
            ... con't

```

Figure 8.36 VHDL code for a Mealy machine

```

        WHEN B =>
            IF w = '0' THEN y <= A ;
            ELSE y <= B ;
            END IF ;
        END CASE ;
    END IF ;
END PROCESS ;

PROCESS ( y, w )
BEGIN
    CASE y IS
        WHEN A =>
            z <= '0' ;
        WHEN B =>
            z <= w ;
        END CASE ;
    END PROCESS ;
END Behavior ;

```

Figure 8.36b VHDL code for a Mealy machine (con't)

 


Figure 8.37 Simulation results for the Mealy machine



 


Figure 8.38 Potential problem with asynchronous inputs to a Mealy FSM

Exemplo – somador serial - MEALY

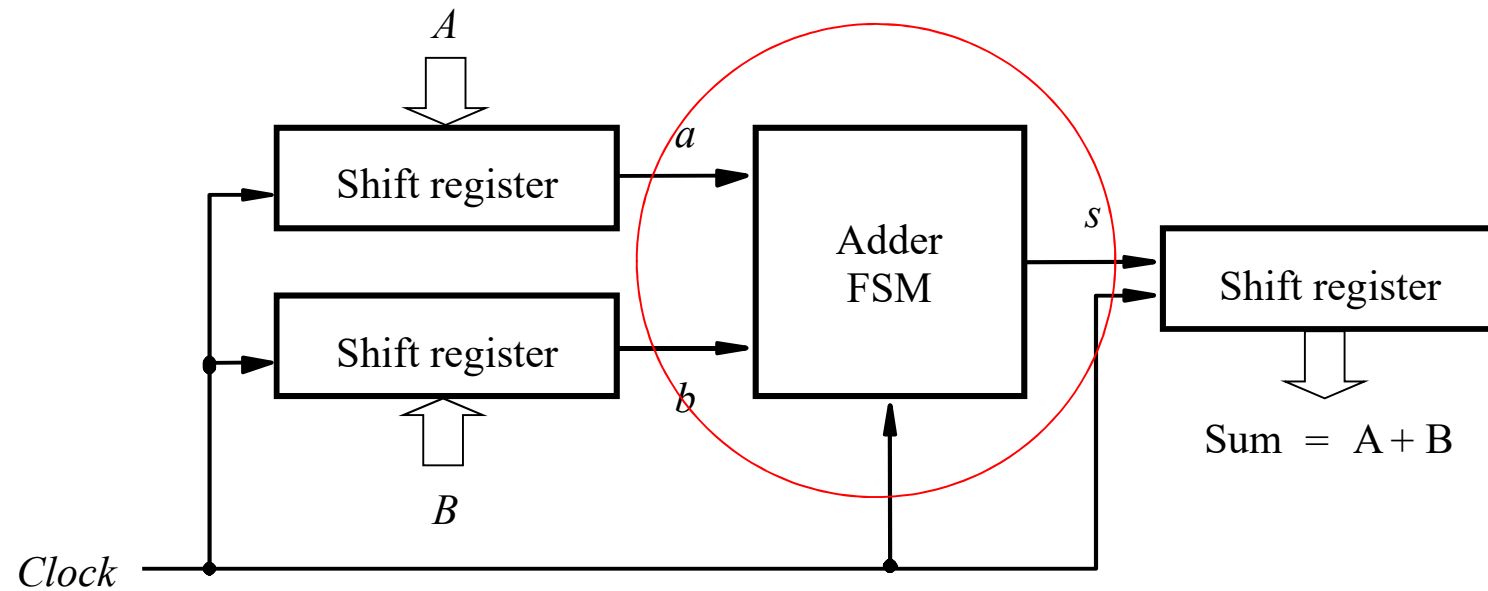

 
Somador serial – diagrama de estados - Mealy



G: carry-in = 0

H: carry-in = 1

 Somador serial – Tabela de estados - Mealy



G: carry-in = 0

H: carry-in = 1

Present state	Next state				Output s			
	$ab=00$	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1

Somador serial – Tabela de estados assinalados - Mealy

Present state y	Next state				Output			
	$ab=00$	01	10	11	00	01	10	11
	Y				s			
0	0	0	0	1	0	1	1	0
1	0	1	1	1	1	0	0	1

ab	00	01	11	10
y				
0	0	0	1	0
1	0	1	1	1

$$Y = ab + ay + by$$

ab	00	01	11	10
y				
0	0	1	0	1
1	1	0	1	0


$$\begin{aligned}
 s &= a'b'y + a'by' + aby + ab'y' = \\
 &= a \text{ xor } b \text{ xor } y
 \end{aligned}$$

Somador serial – Tabela de estados assinalados - Mealy


Present state y	Next state				Output			
	$ab=00$	01	10	11	00	01	10	11
	Y				s			
0	0	0	0	1	0	1	1	0
1	0	1	1	1	1	0	0	1

$$\begin{array}{l}
 \text{carry out} \\
 \nearrow \\
 Y = a b + a y + b y \\
 \searrow \\
 \text{soma}
 \end{array}
 \left. \begin{array}{l}
 Y = a b + a y + b y \\
 s = a \oplus b \oplus y
 \end{array} \right\} \longrightarrow \text{Full adder}$$


Somador serial – Mealy FSM

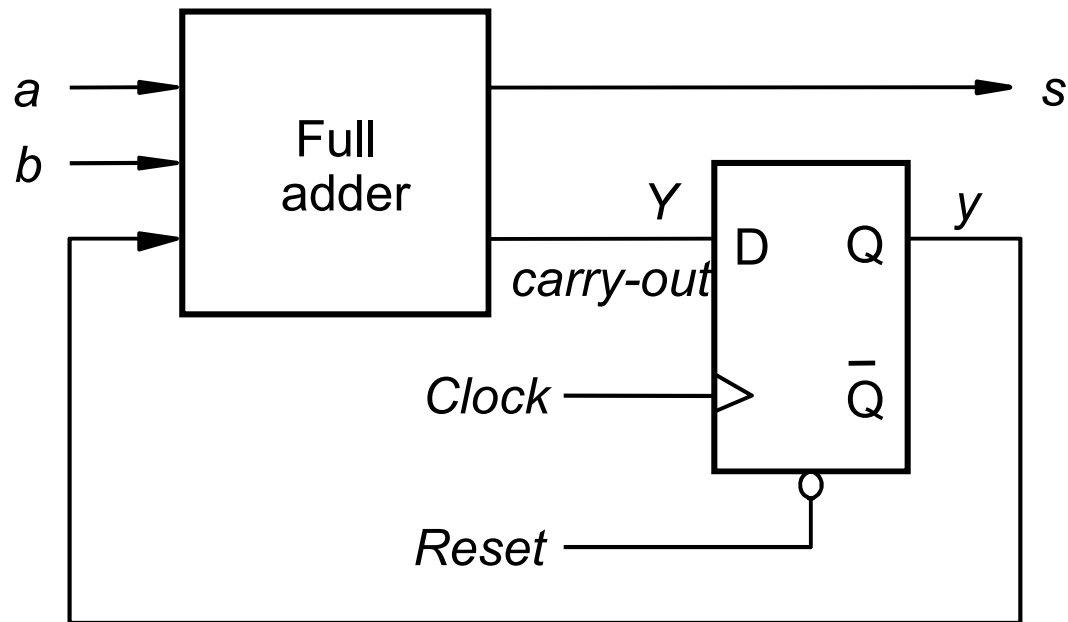


Exemplo – somador serial - MOORE

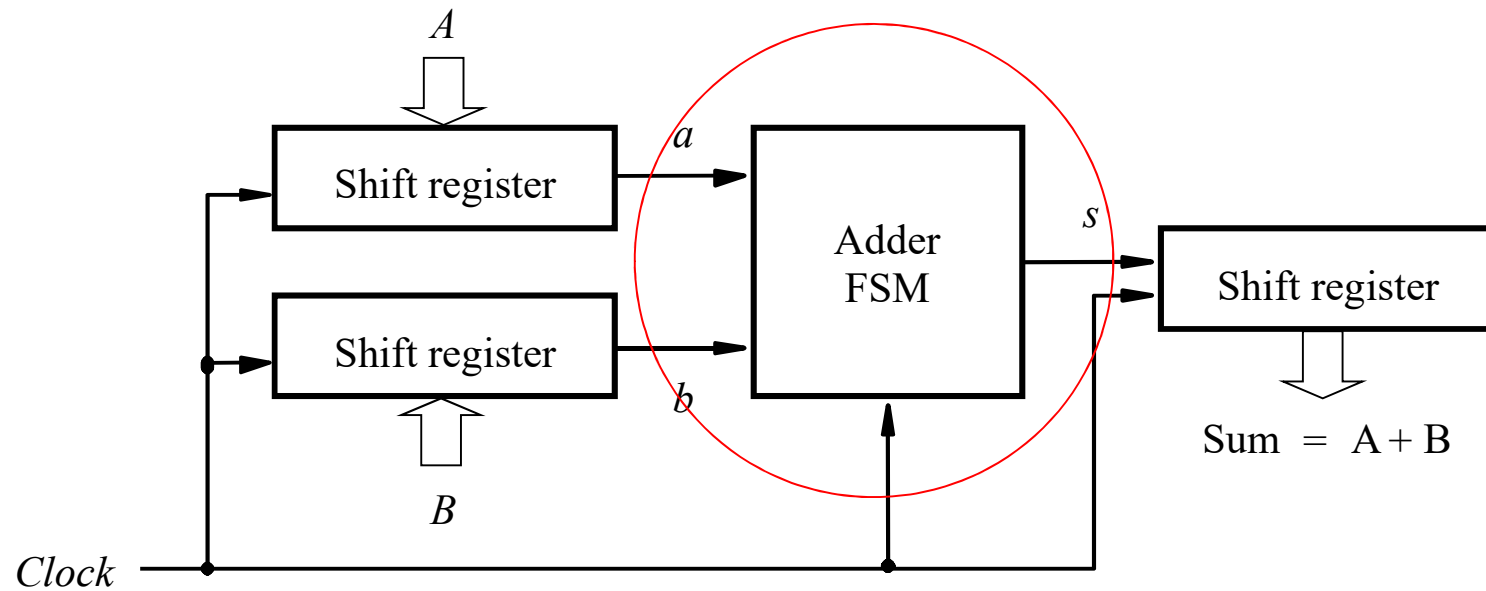

 Somador serial – diagrama de estados - Moore



 Somador serial – tabela de estados - Moore



Present state	Nextstate				Output <i>s</i>
	<i>ab</i> = 00	01	10	11	
G ₀	G ₀	G ₁	G ₁	H ₀	0
G ₁	G ₀	G ₁	G ₁	H ₀	1
H ₀	G ₁	H ₀	H ₀	H ₁	0
H ₁	G ₁	H ₀	H ₀	H ₁	1

Somador serial – tabela de estados assinalados - Moore

Present state y_2y_1	Nextstate				Output s
	$ab=00$	01	10	11	
	Y_2Y_1				
00	0 0	01	0 1	10	0
01	0 0	01	0 1	10	1
10	0 1	10	1 0	11	0
11	0 1	10	1 0	11	1

$y_2 y_1$	00	01	11	10
ab				
00	0	0	1	1
01	1	1	0	0
11	0	0	1	1
10	1	1	0	0

$y_2 y_1$	00	01	11	10
ab				
00	0	0	0	0
01	0	0	1	1
11	1	1	1	1
10	0	0	1	1

y_1	0	1
y_2		
0	0	1
1	0	1


$$s = y_1$$

$$Y_1 = ab'y_2' + a'by_2' + a'b'y_2 + aby_2$$


$$Y_2 = ab + by_2 + ay_2$$


Somador serial – tabela de estados assinalados - Moore

Present state y_2y_1	Nextstate				Output s
	$ab=00$	01	10	11	
	Y_2Y_1				
00	0 0	01	0 1	10	0
01	0 0	01	0 1	10	1
10	0 1	10	1 0	11	0
11	0 1	10	1 0	11	1

 


Somador serial –Moore FSM

 

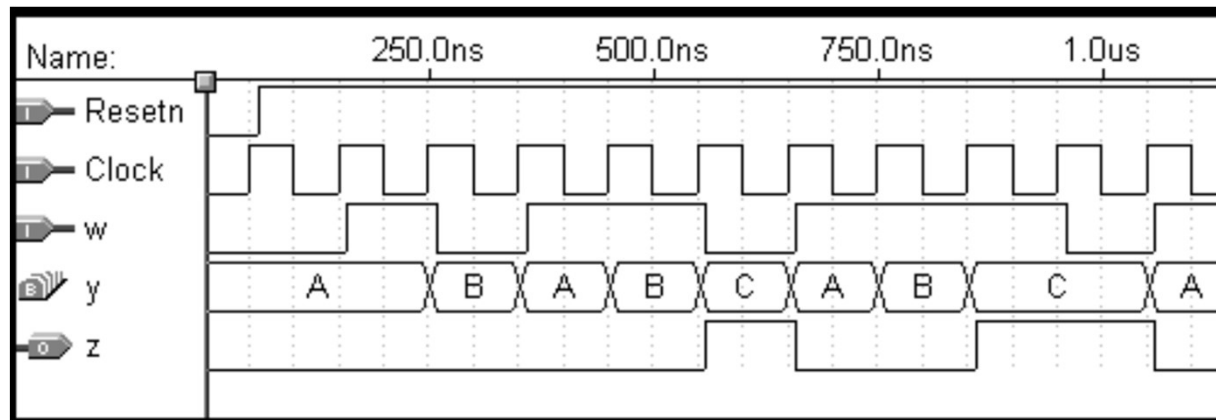

(a) Timing simulation results

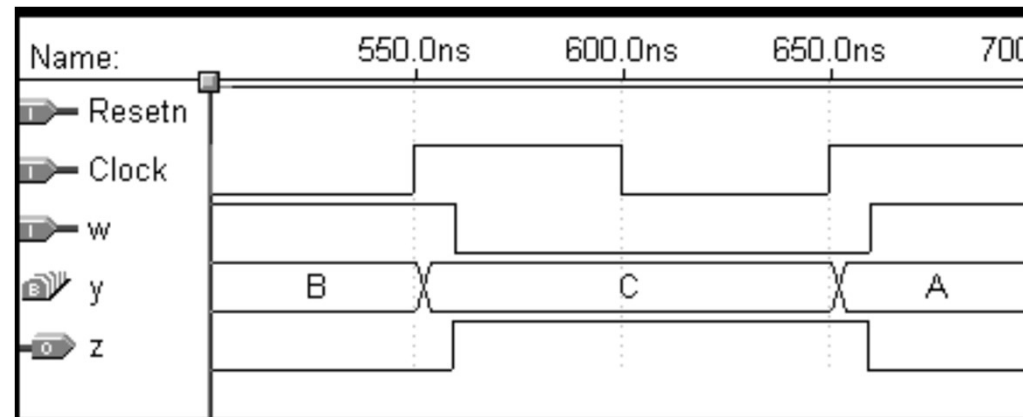

(b) Magnified simulation results, showing timing details

Figure 8.32 Simulation results

(ENTITY declaration not shown)

ARCHITECTURE Behavior OF simple IS

 TYPE State_type IS (A, B, C) ;

 SIGNAL y_present, y_next : State_type ;

BEGIN

 PROCESS (w, y_present)

 BEGIN

 CASE y_present IS

 WHEN A =>

 IF w = '0' THEN

 y_next <= A ;

 ELSE

 y_next <= B ;

 END IF ;

 WHEN B =>

 IF w = '0' THEN

 y_next <= A ;

 ELSE

 y_next <= C ;

 END IF ;

Figure 8.33a Alternative style of code for an FSM

```

        WHEN C =>
            IF w = '0' THEN
                y_next <= A ;
            ELSE
                y_next <= C ;
            END IF ;
        END CASE ;
    END PROCESS ;

PROCESS (Clock, Resetn)
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;

z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;

```

Figure 8.33b Alternative style of code for an FSM (con't)

(ENTITY declaration not shown)

ARCHITECTURE Behavior OF simple IS

TYPE State_TYPE IS (A, B, C);

ATTRIBUTE ENUM ENCODING : STRING ;

ATTRIBUTE ENUM_ENCODING OF State_type : TYPE IS "00 01 11" ;

SIGNAL y_present, y_next : State_type ;

BEGIN

con't ...

Figure 8.34 A user-defined attribute for manual state assignment


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY simple IS
    PORT (   Clock, Reseth, w      : IN  STD_LOGIC ;
            z                      : OUT  STD_LOGIC ) ;
END simple ;

ARCHITECTURE Behavior OF simple IS
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);
    CONSTANT A : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00" ;
    CONSTANT B : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01" ;
    CONSTANT C : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11" ;
BEGIN
    PROCESS ( w, y_present )
    BEGIN
        CASE y_present IS
            WHEN A =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= B ;
                END IF ;

... con't

```

Figure 8.35a Using constants for manual state assignment

```

        WHEN B =>
            IF w = '0' THEN y_next <= A ;
            ELSE y_next <= C ;
            END IF ;
        WHEN C =>
            IF w = '0' THEN y_next <= A ;
            ELSE y_next <= C ;
            END IF ;
        WHEN OTHERS =>
            y_next <= A ;
    END CASE ;
END PROCESS ;

PROCESS ( Clock, Resetn )
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;
z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;

```

Figure 8.35b Using constants for manual state assignment (cont')

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mealy IS
    PORT ( Clock, Resetn, w      : IN    STD_LOGIC ;
          z                      : OUT   STD_LOGIC ) ;
END mealy ;

ARCHITECTURE Behavior OF mealy IS
    TYPE State_type IS (A, B) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            y <= A ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            CASE y IS
                WHEN A =>
                    IF w = '0' THEN y <= A ;
                    ELSE y <= B ;
                    END IF ;
            ... con't

```

Figure 8.36 VHDL code for a Mealy machine

```

        WHEN B =>
            IF w = '0' THEN y <= A ;
            ELSE y <= B ;
            END IF ;
        END CASE ;
    END IF ;
END PROCESS ;

PROCESS ( y, w )
BEGIN
    CASE y IS
        WHEN A =>
            z <= '0' ;
        WHEN B =>
            z <= w ;
        END CASE ;
    END PROCESS ;
END Behavior ;

```

Figure 8.36b VHDL code for a Mealy machine (con't)

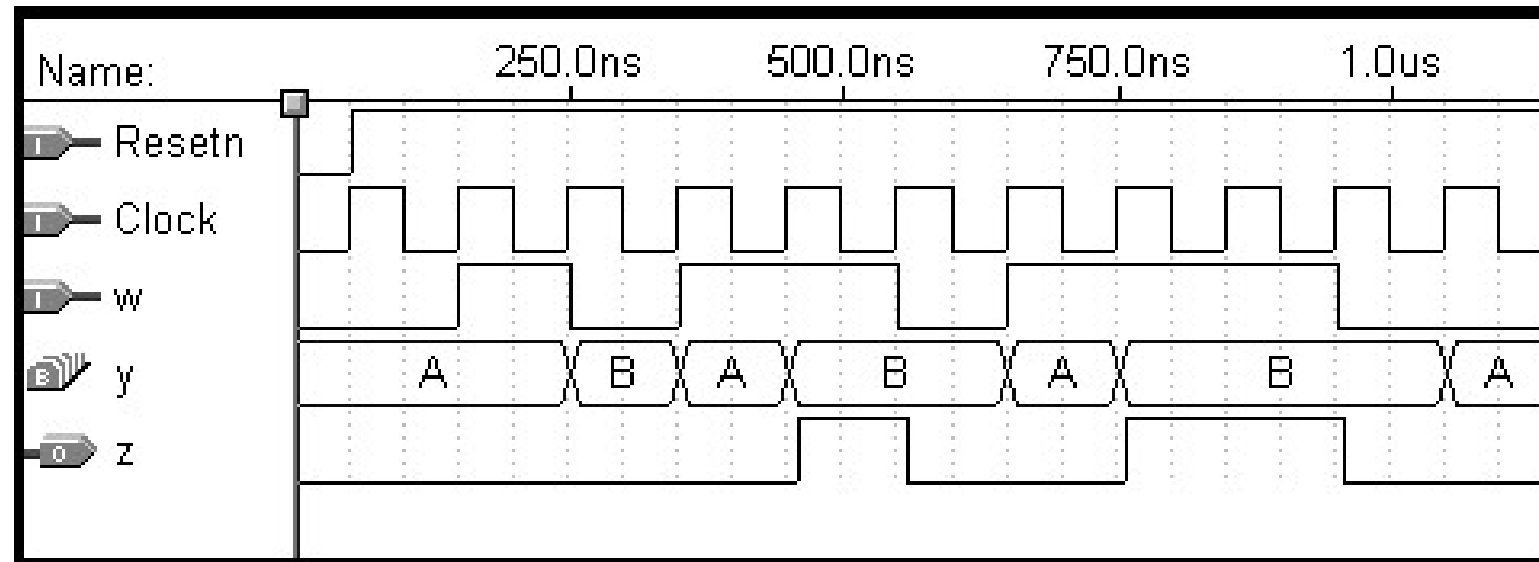


Figure 8.37 Simulation results for the Mealy machine

 


Figure 8.38 Potential problem with asynchronous inputs to a Mealy FSM

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
-- left-to-right shift register with parallel load and enable
ENTITY shiftrne IS
    GENERIC ( N : INTEGER := 4 ) ;
    PORT ( R      : IN          STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
           L, E, w : IN          STD_LOGIC ;
           Clock   : IN          STD_LOGIC ;
           Q       : BUFFER      STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
END shiftrne ;
ARCHITECTURE Behavior OF shiftrne IS
BEGIN
    PROCESS
    BEGIN

... con't

```

Figure 8.48a Code for a left-to-right shift register with an enable input

```

WAIT UNTIL Clock'EVENT AND Clock = '1' ;
IF E = '1' THEN
    IF L = '1' THEN
        Q <= R ;
    ELSE
        Genbits: FOR i IN 0 TO N-2 LOOP
            Q(i) <= Q(i+1) ;
        END LOOP ;
        Q(N-1) <= w ;
    END IF ;
END IF ;
END PROCESS ;
END Behavior ;

```

Figure 8.48b Code for a left-to-right shift register with an enable input (con't)


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY serial IS
    GENERIC ( length : INTEGER := 8 ) ;
    PORT (   Clock      : IN          STD_LOGIC ;
            Reset       : IN          STD_LOGIC ;
            A, B        : IN          STD_LOGIC_VECTOR(length-1 DOWNTO 0) ;
            Sum         : BUFFER      STD_LOGIC_VECTOR(length-1 DOWNTO 0) );
END serial ;

ARCHITECTURE Behavior OF serial IS
    COMPONENT shiftrne
        GENERIC ( N : INTEGER := 4 ) ;
        PORT (   R          : IN          STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
                L, E, w     : IN          STD_LOGIC ;
                Clock       : IN          STD_LOGIC ;
                Q           : BUFFER      STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
    END COMPONENT ;
    SIGNAL QA, QB, Null_in : STD_LOGIC_VECTOR(length-1 DOWNTO 0) ;
    SIGNAL s, Low, High, Run : STD_LOGIC ;
    SIGNAL Count : INTEGER RANGE 0 TO length ;
    TYPE State_type IS (G, H) ;
    SIGNAL y : State_type ;

```

... con't

Figure 8.49a VHDL code for the serial adder

BEGIN

Low <= '0' ; High <= '1' ;

ShiftA: shiftrne GENERIC MAP (N => length)

PORT MAP (A, Reset, High, Low, Clock, QA) ;

ShiftB: shiftrne GENERIC MAP (N => length)

PORT MAP (B, Reset, High, Low, Clock, QB) ;

AdderFSM: PROCESS (Reset, Clock)

BEGIN

IF Reset = '1' THEN

y <= G ;

ELSIF Clock'EVENT AND Clock = '1' THEN

CASE y IS

WHEN G =>

IF QA(0) = '1' AND QB(0) = '1' THEN y <= H ;

ELSE y <= G ;

END IF ;

WHEN H =>

IF QA(0) = '0' AND QB(0) = '0' THEN y <= G ;

ELSE y <= H ;

END IF ;

END CASE ;

END IF ;

END PROCESS AdderFSM ;

... con't

Figure 8.49b VHDL code for the serial adder (con't)

```

WITH y SELECT
    s <= QA(0) XOR QB(0) WHEN G,
        NOT ( QA(0) XOR QB(0) ) WHEN H ;
Null_in <= (OTHERS => '0') ;
ShiftSum: shiftrne GENERIC MAP ( N => length )
    PORT MAP ( Null_in, Reset, Run, s, Clock, Sum ) ;
Stop: PROCESS
BEGIN
    WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
    IF Reset = '1' THEN
        Count <= length ;
    ELSIF Run = '1' THEN
        Count <= Count -1 ;
    END IF ;
END PROCESS ;
Run <= '0' WHEN Count = 0 ELSE '1' ; -- stops counter and ShiftSum
END Behavior ;

```

Figure 8.49c VHDL code for the serial adder (con't)

Minimização de estados

Definição 1 – Sejam 2 estados S_i e S_j . Eles são ditos equivalentes se somente se para todas as possíveis sequências de entradas, a mesma sequência de saída é produzida, Levando para o mesmo estado ou para estados equivalentes.

OBS – É mais fácil mostrar os estados que não são equivalentes.

Procedimento de Particionamento

1. Separar em blocos, onde os estados com mesma saída devam pertencer ao bloco
2. Verificar os sucessores para cada combinação de entrada. Se estes sucessores pertencerem a um determinado subconjunto, deixá-lo no subconjunto, senão, criar outro subconjunto com estes estados.
3. Repetir até conseguir um resultado igual ao anterior.

Minimização de estados

Tabela de Estados

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

Minimização de estados

Tabela de Estados

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

P1 = (ABCDEFGG)

P2 = (ABD) (CEFG)

→ próximos estados para $w = 0$ (BDB) (FFEF)
 → próximos estados para $w = 1$ (CFG) (ECDG)

P3 = (ABD) (CEG) (F)

→ próximos estados para $w = 0$ (BDB) (FFF) (E)
 → próximos estados para $w = 1$ (CFG) (ECG) (D)

P4 = (AD) (B) (CEG) (F)

→ próximos estados para $w = 0$ (BB) (D) (FFF) (E)
 → próximos estados para $w = 1$ (CG) (F) (ECG) (D)

P5 = (AD) (B) (CEG) (F)

→ FIM

Minimização de estados

Tabela de Estados

Present state	Next state		Output z
	w = 0	w = 1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

Present state	Next state		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

P1 = (ABCDEFGG)

P2 = (ABD) (CEFG)

P3 = (ABD) (CEG) (F)

P4 = (AD) (B) (CEG) (F)

P5 = (AD) (B) (CEG) (F)

→ próximos estados para w = 0

→ próximos estados para w = 1

→ próximos estados para w = 0

→ próximos estados para w = 1

→ próximos estados para w = 0

→ próximos estados para w = 1

→ FIM

(BDB) (FFEF)

(CFG) (ECDG) - D não pertence ao grupo de C E G

(BDB) (FFF) (E)

(CFG) (ECG) (D) - F não pertence ao grupo C G

(BB) (D) (FFF) (D)

(CG) (F) (ECG) (D)

Example 8.6

As another example of minimization, we will consider the design of a sequential circuit that could control a vending machine. Suppose that a coin-operated vending machine dispenses candy under the following conditions:

- The machine accepts nickels and dimes.
- It takes 15 cents for a piece of candy to be released from the machine.
- If 20 cents is deposited, the machine will not return the change, but it will credit the buyer with 5 cents and wait for the buyer to make a second purchase.

All electronic signals in the vending machine are synchronized to the positive edge of a clock signal, named *Clock*. The exact frequency of the clock signal is not important for our example, but we will assume a clock period of 100 ns. The vending machine's coin-receptor mechanism generates two signals, $sense_D$ and $sense_N$, which are asserted when a dime or a nickel is detected. Because the coin receptor is a mechanical device and thus very slow compared to an electronic circuit, inserting a coin causes $sense_D$ or $sense_N$ to be set to 1 for a large number of clock cycles. We will assume that the coin receptor also generates two other signals, named *D* and *N*. The *D* signal is set to 1 for one clock cycle after $sense_D$ becomes 1, and *N* is set to 1 for one clock cycle after $sense_N$ becomes 1. The timing relationships between *Clock*, $sense_D$, $sense_N$, *D*, and *N* are illustrated in Figure 8.53a. The hash marks on the waveforms indicate that $sense_D$ or $sense_N$ may be 1 for many clock cycles. Also, there may be an arbitrarily long time between the insertion of two consecutive coins. Note that since the coin receptor can accept only one coin at a time, it is not possible to have both *D* and *N* set to 1 at once. Figure 8.53b illustrates how the *N* signal may be generated from the $sense_N$ signal.

Máquina de Moore, cujas entradas são N(5) e D(10), saída z que, quando = 1, libera o produto.


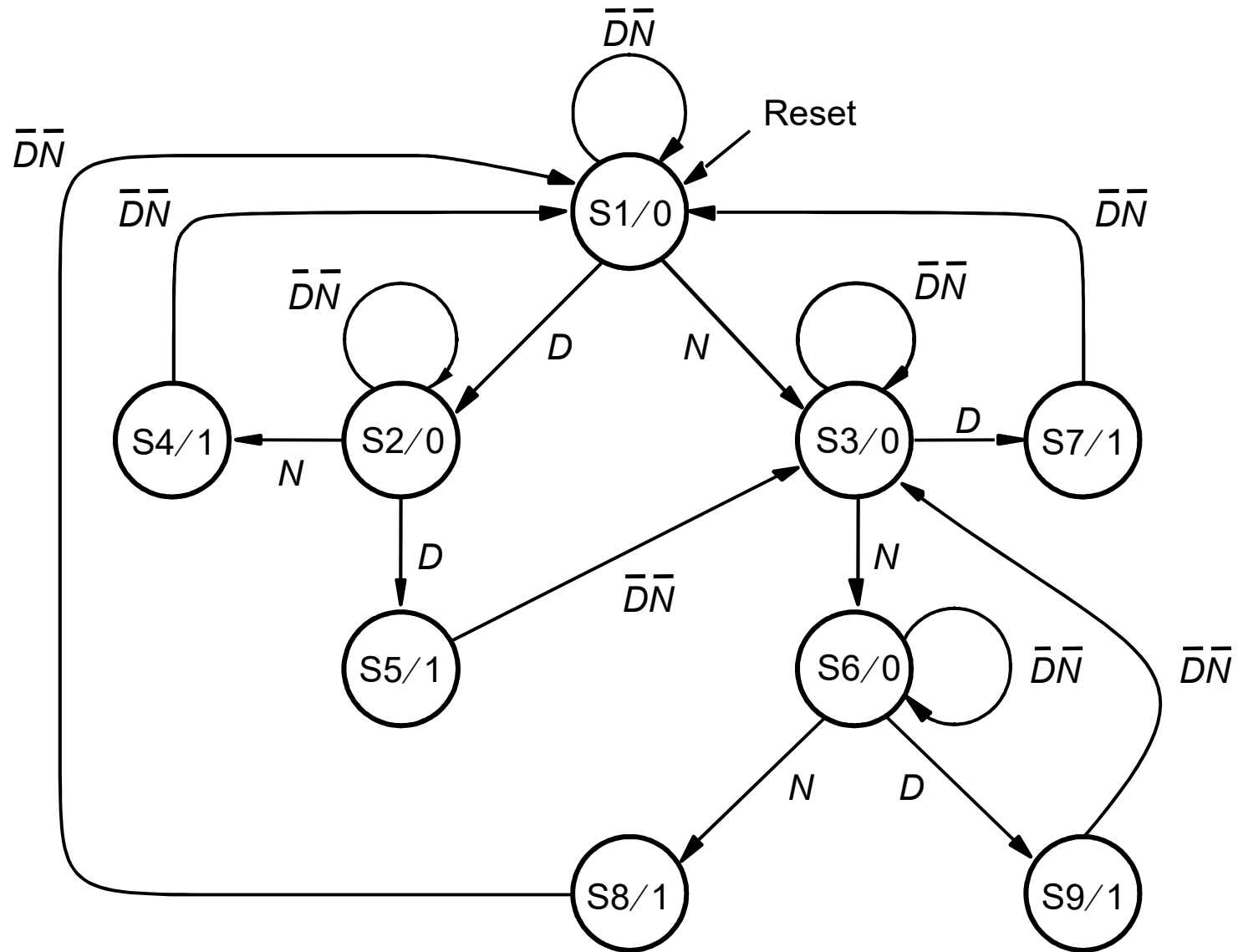


Figure 8.54 State diagram for Example 8.6

Present state	Next state				Output z
	$DN = 00$	01	10	11	
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S6	S7	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1
S6	S6	S8	S9	—	0
S7	S1	—	—	—	1
S8	S1	—	—	—	1
S9	S3	—	—	—	1

Figura 8.55 Tabela de Estados -
Exemplo 8.6

Present state	Next state				Output z
	$DN=00$	01	10	11	
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S6	S7	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1
S6	S6	S8	S9	—	0
S7	S1	—	—	—	1
S8	S1	—	—	—	1
S9	S3	—	—	—	1

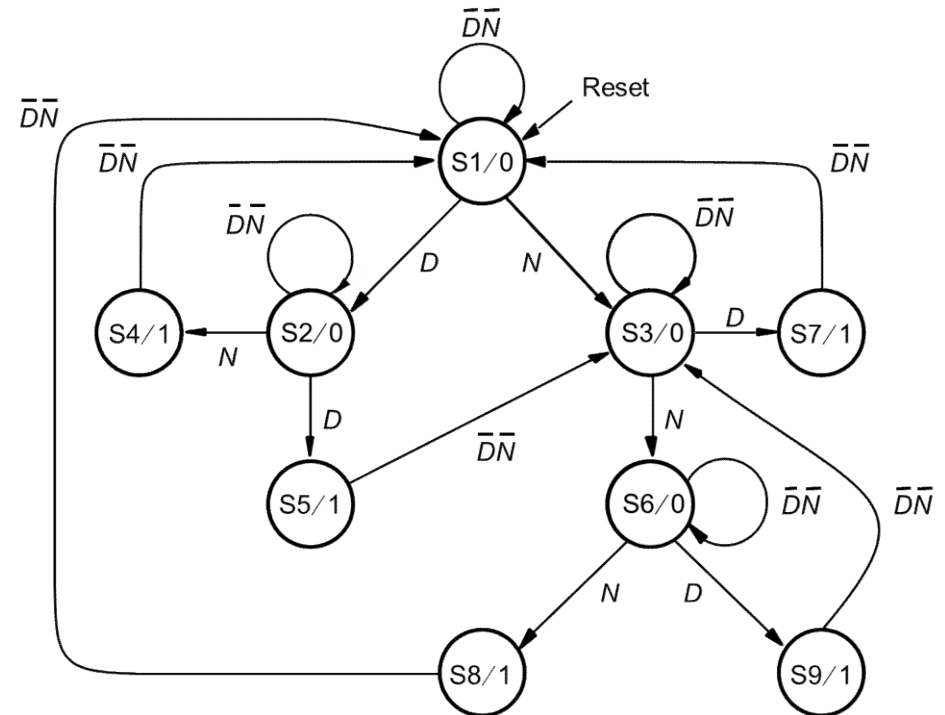

Present state	Next state				Output z
	$DN = 00$	01	10	11	
S1	S1	S3	S2	–	0
S2	S2	S4	S5	–	0
S3	S3	S6	S7	–	0
S4	S1	–	–	–	1
S5	S3	–	–	–	1
S6	S6	S8	S9	–	0
S7	S1	–	–	–	1
S8	S1	–	–	–	1
S9	S3	–	–	–	1

P1 = (S1S2S3S4S5S6S7S8S9)

P2 = (S1 S2 S3 S6) (S4 S5 S7 S8 S9) → SUCESSORES 00 (S1 S2 S3 S6) (S1 S3 S1 S1 S3)
→ SUCESSORES 01 (S3 S4 S6 S8) (- - - - -)
→ SUCESSORES 10 (S2 S5 S7 S9) (- - - - -)
→ SUCESSORES 11 (- - - -) (- - - - -)

P3 = (S1 S3) (S2 S6) (S4 S5 S7 S8 S9) → SUCESSORES 00 (S1 S3) (S2 S6) (S1 S3 S1 S1 S3)
→ SUCESSORES 01 (S3 S6) (S4 S8) (- - - - -)
→ SUCESSORES 10 (S2 S7) (S5 S9) (- - - - -)
→ SUCESSORES 11 (- -) (- -) (- - - - -)

P4 = (S1) (S3) (S2 S6) (S4 S5 S7 S8 S9) → SUCESSORES 00 (S1) (S3) (S2 S6) (S1 S3 S1 S1 S3)
→ SUCESSORES 01 (S3) (S6) (S4 S8) (- - - - -)
→ SUCESSORES 10 (S2) (S7) (S5 S9) (- - - - -)
→ SUCESSORES 11 (-) (-) (- -) (- - - - -)

P5 = (S1) (S3) (S2 S6) (S4 S7 S8) (S5 S9) → SUCESSORES 00 (S1) (S3) (S2 S6) (S1 S1 S1) (S3 S3)
→ SUCESSORES 01 (S3) (S6) (S4 S8) (- - - - -)
→ SUCESSORES 10 (S2) (S7) (S5 S9) (- - - - -)
→ SUCESSORES 11 (-) (-) (- -) (- - - - -)

P6 = (S1) (S3) (S2 S6) (S4 S7 S8) (S5 S9)

Present state	Next state				Output z
	$DN = 00$	01	10	11	
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S6	S7	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1
S6	S6	S8	S9	—	0
S7	S1	—	—	—	1
S8	S1	—	—	—	1
S9	S3	—	—	—	1

Present state $y_3y_2y_1$	Next state $Y_3Y_2Y_1$				Output z
	DN 00	01	10	11	
S1 000	S1 000	S3 010	S2 001	—	0
S2 001	S2 001	S4 011	S5 100	—	0
S3 010	S3 010	S2 001	S4 011	—	0
S4 011	S1 000	—	—	—	1
S5 100	S3 010	—	—	—	1

Figure 8.56 Minimized state table for Example 8.6

Present state y3y2y1	Next state Y3Y2Y1				Output z
	00	<i>DN</i> 01	10	11	
S1 000	S1 000	S3 010	S2 001	—	0
S2 001	S2 001	S4 011	S5 100	—	0
S3 010	S3 010	S2 001	S4 011	—	0
S4 011	S1 000	—	—	—	1
S5 100	S3 010	—	—	—	1

$$Y3 = y1.D$$

y3 y2	00	01	11	10
y1 D				
00	0	0	d	0
01	0	0	d	d
11	1	d	d	d
10	0	0	d	d

$$N=0$$

y3 y2	00	01	11	10
y1 D				
00	0	0	d	d
01	d	d	d	d
11	d	d	d	d
10	0	d	d	d

$$N=1$$

Figure 8.56 Minimized state table for Example 8.6

Present state y ₃ y ₂ y ₁	Next state Y ₃ Y ₂ Y ₁				Output z
	00	01	10	11	
S1 000	S1 000	S3 010	S2 001	—	0
S2 001	S2 001	S4 011	S5 100	—	0
S3 010	S3 010	S2 001	S4 011	—	0
S4 011	S1 000	—	—	—	1
S5 100	S3 010	—	—	—	1

$$Y_2 = N y'_2 + y_3 y'_2 + N y_2 y'_1$$

y ₃ y ₂	00	01	11	10
y ₁ D				
00	0	1	d	1
01	0	1	d	d
11	0	d	d	d
10	0	0	d	d

N=0

y ₃ y ₂	00	01	11	10
y ₁ D				
00	1	0	d	d
01	d	d	d	d
11	d	d	d	d
10	1	d	d	d

N=1

Figure 8.56 Minimized state table for Example 8.6

Present state y3y2y1	Next state Y3Y2Y1				Output z
	00	01	10	11	
S1 000	S1 000	S3 010	S2 001	—	0
S2 001	S2 001	S4 011	S5 100	—	0
S3 010	S3 010	S2 001	S4 011	—	0
S4 011	S1 000	—	—	—	1
S5 100	S3 010	—	—	—	1

$$Y1 = y'3y2 + y3 N + y'2y1 N'$$

y3 y2	00	01	11	10
y1 D				
00	0	0	d	0
01	1	1	d	d
11	0	d	d	d
10	1	0	d	d

N=0

y3 y2	00	01	11	10
y1 D				
00	0	1	d	d
01	d	d	d	d
11	d	d	d	d
10	1	d	d	d

N=1


Figure 8.56 Minimized state table for Example 8.6

Present state y3y2y1	Next state Y3Y2Y1				Output z
	00	<i>DN</i> 01	10	11	
S1 000	S1 000	S3 010	S2 001	—	0
S2 001	S2 001	S4 011	S5 100	—	0
S3 010	S3 010	S2 001	S4 011	—	0
S4 011	S1 000	—	—	—	1
S5 100	S3 010	—	—	—	1


$$z = y_3$$

y3 y2	00	01	11	10
y1				
0	0	0	d	1
1	0	0	d	d

Figure 8.56 Minimized state table for Example 8.6

 

(a) Timing diagram

 

(b) Circuit that generates *N*

Figure 8.53 Signals for the vending machine

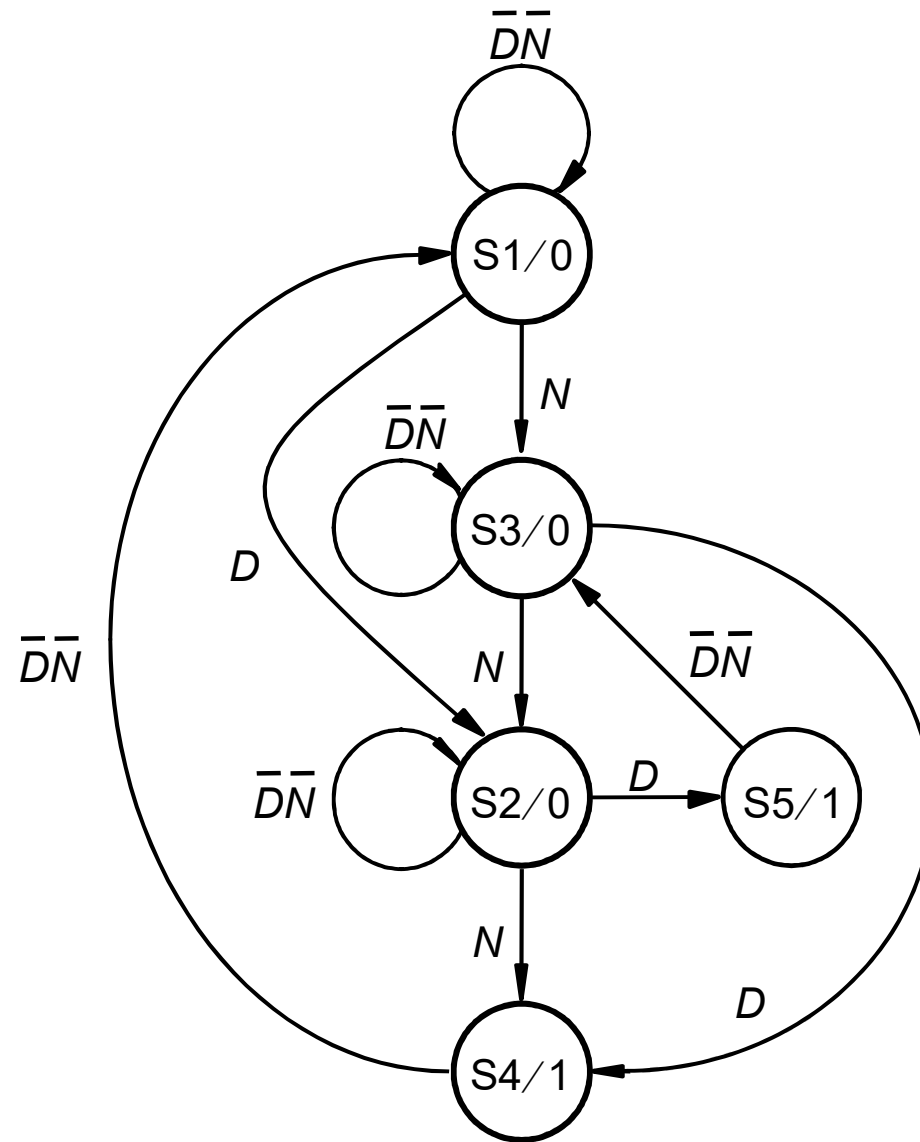


Figure 8.57 Minimized state diagram for Example 8.6

Example 8.6

As another example of minimization, we will consider the design of a sequential circuit that could control a vending machine. Suppose that a coin-operated vending machine dispenses candy under the following conditions:

- The machine accepts nickels and dimes.
- It takes 15 cents for a piece of candy to be released from the machine.
- If 20 cents is deposited, the machine will not return the change, but it will credit the buyer with 5 cents and wait for the buyer to make a second purchase.

All electronic signals in the vending machine are synchronized to the positive edge of a clock signal, named *Clock*. The exact frequency of the clock signal is not important for our example, but we will assume a clock period of 100 ns. The vending machine's coin-receptor mechanism generates two signals, $sense_D$ and $sense_N$, which are asserted when a dime or a nickel is detected. Because the coin receptor is a mechanical device and thus very slow compared to an electronic circuit, inserting a coin causes $sense_D$ or $sense_N$ to be set to 1 for a large number of clock cycles. We will assume that the coin receptor also generates two other signals, named *D* and *N*. The *D* signal is set to 1 for one clock cycle after $sense_D$ becomes 1, and *N* is set to 1 for one clock cycle after $sense_N$ becomes 1. The timing relationships between *Clock*, $sense_D$, $sense_N$, *D*, and *N* are illustrated in Figure 8.53a. The hash marks on the waveforms indicate that $sense_D$ or $sense_N$ may be 1 for many clock cycles. Also, there may be an arbitrarily long time between the insertion of two consecutive coins. Note that since the coin receptor can accept only one coin at a time, it is not possible to have both *D* and *N* set to 1 at once. Figure 8.53b illustrates how the *N* signal may be generated from the $sense_N$ signal.

Máquina de Mealy, cujas entradas são N(5) e D(10), saída z que, quando = 1, libera o produto.

 


Figure 8.58 Mealy-type FSM for Example 8.6

ESTADO ATUAL	PRÓXIMO ESTADO - Y1Y2				SAÍDAS - z			
y1y2	D'N'	D'N	DN'	DN	D'N'	D'N	DN'	DN
S1 00	S1 0 0	S3 1 0	S2 0 1	NN	0	0	0	NN
S2 01	S2 0 1	S1 0 0	S3 1 0	NN	0	1	1	NN
S3 10	S3 1 0	S2 0 1	S1 0 0	NN	0	0	1	NN

$$Y1 = y1D'N' + y1'y2'N + y2D$$

y1y2/				
DN	00	01	11	10
00	0	0	d	1
01	1	0	d	0
11	d	d	d	d
10	0	1	d	0

$$Y2 = y1'y2'D + y2D'N' + y1N$$

y1y2/				
DN	00	01	11	10
00	0	1	d	0
01	0	0	d	1
11	d	d	d	d
10	1	0	d	0

$$z = y2N + y2D + y1D$$

y1y2/				
DN	00	01	11	10
00	0	0	d	0
01	0	1	d	0
11	d	d	d	d
10	0	1	d	1

Mealy-type FSM for Example 8.6

Tabela com estados não definidos

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

Figure 8.59 Incompletely specified state table for Example 8.7

Tabela com estados não definidos

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	B	C	0	0
B	D	—	0	—
C	F	E	0	1
D	B	G	0	0
E	F	C	0	1
F	E	D	0	1
G	F	—	0	—

P1 = (ABCDEFGG)

P2 = (AD) (BG) (CEF)

➔ PRÓXIMO ESTADO 0 (BB) (DF) (FFE)

➔ PRÓXIMO ESTADO 1 (CG) (--) (ECD)

P3 = (A) (D) (BG) (CE) (F)

➔ PRÓXIMO ESTADO 0 (B) (B) (DF) (FF) (E)

➔ PRÓXIMO ESTADO 1 (C) (G) (- -) (EC) (D)

P4 = (A) (D) (B) (G) (CE) (F)

➔ PRÓXIMO ESTADO 0 (B) (B) (D) (F) (FF) (E)

➔ PRÓXIMO ESTADO 1 (C) (G) (-) (-) (EC) (D)

P5 = (A) (D) (B) (G) (CE) (F)

➔ FIM

Figure 8.59 Incompletely specified state table for Example 8.7

Contador

Projete um contador módulo 8, síncrono que conta na borda de subida, usando FF tipo D, que tenha uma entrada w , que controla a contagem ($w = 0$ congela e $w = 1$ permite a contagem). Para reiniciar a contagem, um sinal de reset faz com que ele volte a zero. MÁQUINA MOORE

Contador

Projete um contador módulo 8, síncrono que conta na borda de subida, usando FF tipo D, que tenha uma entrada w , que controla a contagem ($w = 0$ congela e $w = 1$ permite a contagem). Para reiniciar a contagem, um sinal de reset faz com que ele volte a zero. MOORE

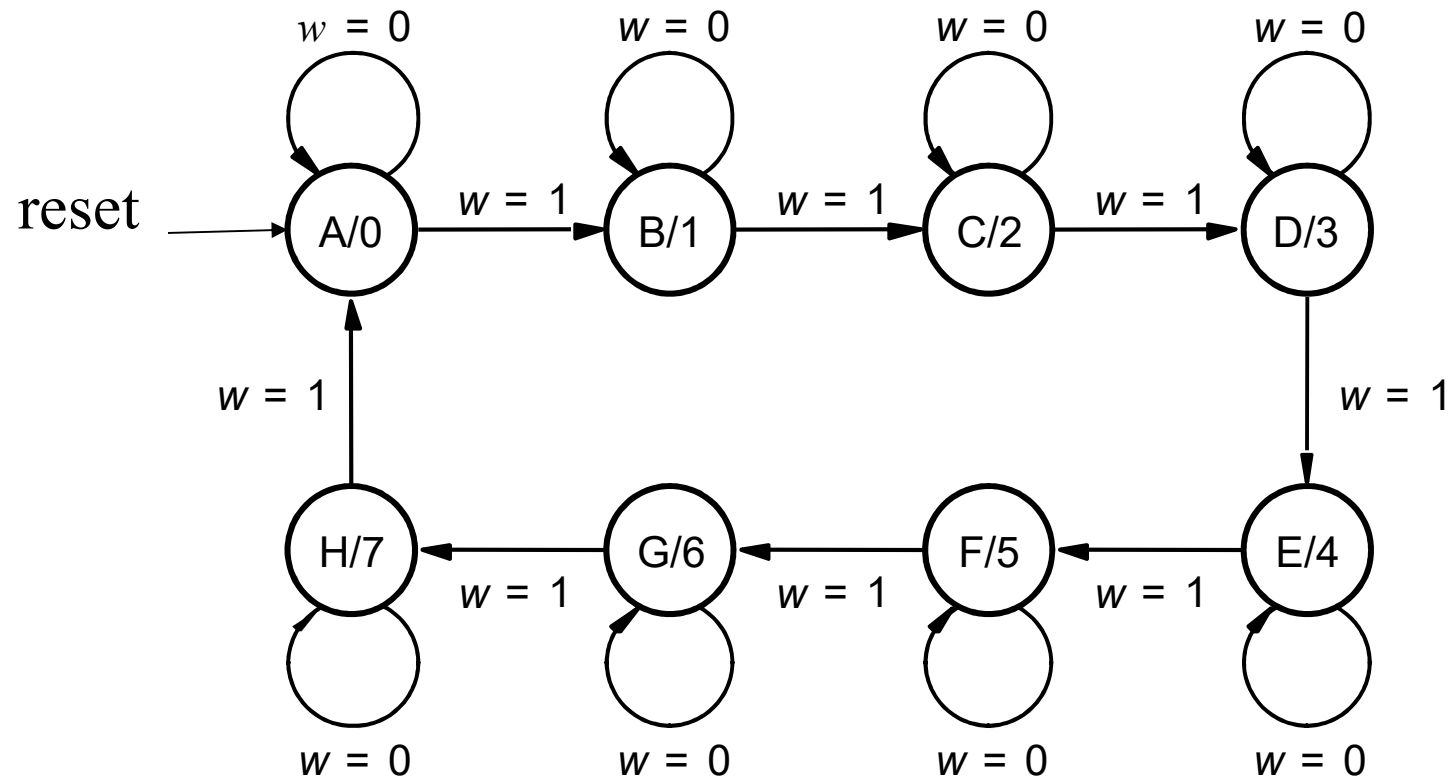



Figure 8.60 State diagram for a counter

Present state	Next state		Output
	$w = 0$	$w = 1$	
A	A	B	0
B	B	C	1
C	C	D	2
D	D	E	3
E	E	F	4
F	F	G	5
G	G	H	6
H	H	A	7


Figure 8.61 State table for the counter

	Present state $y_2y_1y_0$	Next state		Count $z_2z_1z_0$
		$w = 0$	$w = 1$	
		$Y_2Y_1Y_0$	$Y_2Y_1Y_0$	
A	000	000	001	000
B	001	001	010	001
C	010	010	011	010
D	011	011	100	011
E	100	100	101	100
F	101	101	110	101
G	110	110	111	110
H	111	111	000	111


Figure 8.62 State-assigned table for the counter

 

$$Y_0 = \bar{w}y_0 + w\bar{y}_0$$

 

 
$$Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1$$



$$Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2$$

Figure 8.63 Karnaugh maps for D flip-flops for the counter

Diagrama do circuito do contador

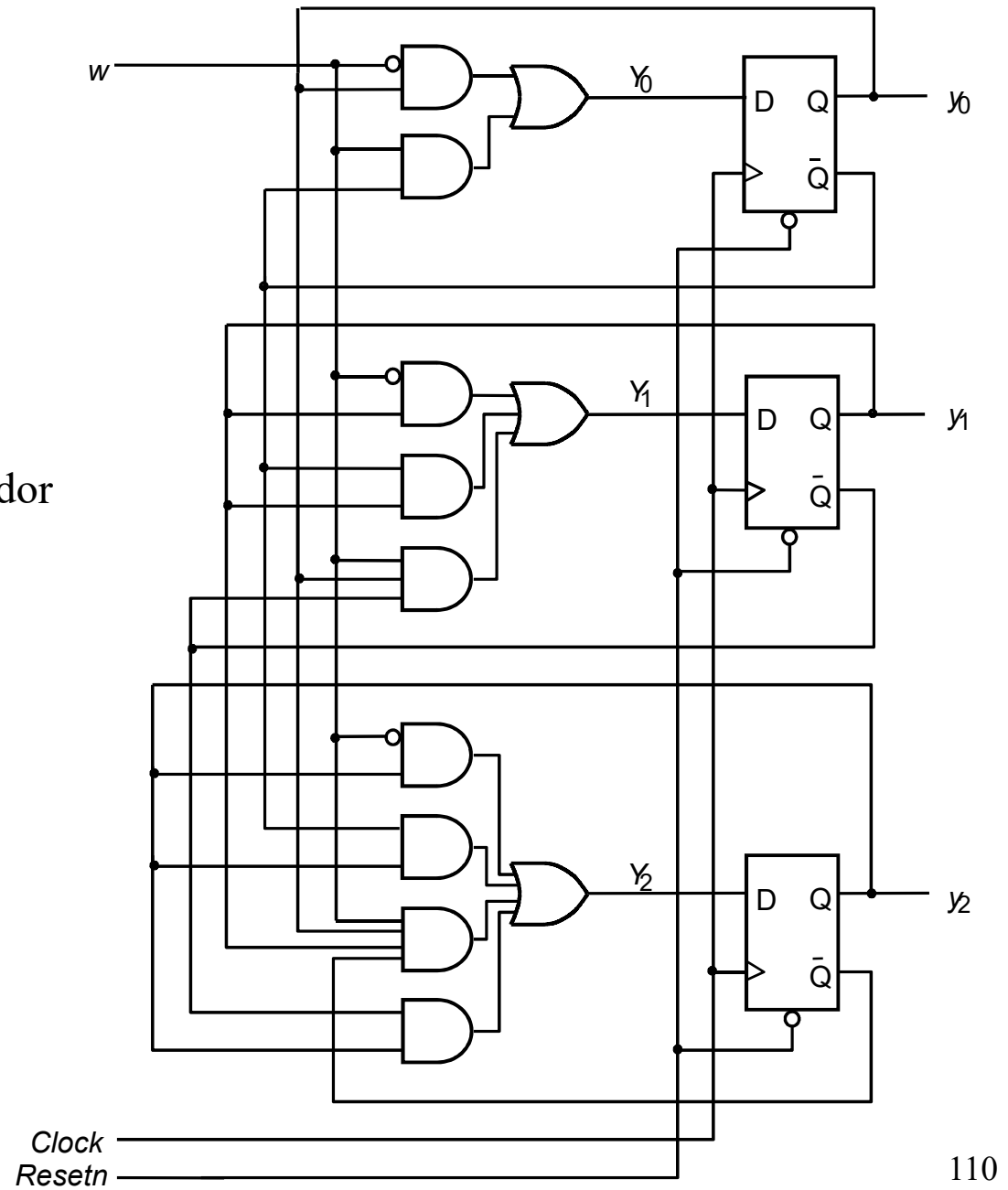


Contador

Projete um contador módulo 8, síncrono que conta na borda de subida, usando FF tipo D, que tenha uma entrada w , que controla a contagem ($w = 0$ congela e $w = 1$ permite a contagem). Para reiniciar a contagem, um sinal de reset faz com que ele volte a zero. MEALY

Contador

 Projete um contador módulo 8, síncrono que conta na borda de subida, usando FF tipo D, que tenha uma entrada w , que controla a contagem ($w = 0$ congela e $w = 1$ permite a contagem). Para reiniciar a contagem, um sinal de reset faz com que ele volte a zero. MEALY



	Present state $y_2y_1y_0$	Next state	
		$w = 0$	$w = 1$
		$Y_2Y_1Y_0$	$Y_2Y_1Y_0$
A	000	000	001
B	001	001	010
C	010	010	011
D	011	011	100
E	100	100	101
F	101	101	110
G	110	110	111
H	111	111	000

MEALY


$z_2z_1z_0$

$w=0$			$w=1$		
z_2	z_1	z_0	z_2	z_1	z_0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Figure 8.62 State-assigned table for the counter

Contador

 Projete um contador módulo 8, síncrono que conta na borda de subida, usando FF tipo D. Para reiniciar a contagem, um sinal de reset faz com que ele volte a zero. MOORE e MEALY



Projete um contador módulo 8, síncrono que conta na borda de subida, usando FF tipo D. Para reiniciar a contagem, um sinal de reset faz com que ele volte a zero. MOORE e MEALY

	Present state $y_2 y_1 y_0$	Next state	Count $z_2 z_1 z_0$
		$Y_2 Y_1 Y_0$	
A	000	001	000
B	001	010	001
C	010	011	010
D	011	100	011
E	100	101	100
F	101	110	101
G	110	111	110
H	111	000	111

FF JK

Quando $J = 0$, $K = d$ e o estado é 0 \rightarrow mantém estado em 0


Quando $J = 1$, $K = d$ e o estado é 0 \rightarrow muda estado para 1

Quando $J = d$, $K = 0$ e o estado é 1 \rightarrow mantém estado para 1

Quando $J = d$, $K = 1$ e o estado é 1 \rightarrow muda estado para 0

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Tabela Verdade

 

(c) Símbolo Gráfico

	Present state $y_2y_1y_0$	Flip-flop inputs								Count $z_2z_1z_0$
		$w = 0$				$w = 1$				
		$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	
A	000	000	0d	0d	0d	001	0d	0d	1d	000
B	001	001	0d	0d	d0	010	0d	1d	d1	001
C	010	010	0d	d0	0d	011	0d	d0	1d	010
D	011	011	0d	d0	d0	100	1d	d1	d1	011
E	100	100	d0	0d	0d	101	d0	0d	1d	100
F	101	101	d0	0d	d0	110	d0	1d	d1	101
G	110	110	d0	d0	0d	111	d0	d0	1d	110
H	111	111	d0	d0	d0	000	d1	d1	d1	111

Figure 8.65 Excitation table for the counter with JK flip-flops

Mapa Karnaugh - contador

		y_1y_0			
		00	01	11	10
wy_2	00	0	d	d	0
	01	0	d	d	0
	11	1	d	d	1
	10	1	d	d	1

$$J_0 = w$$

		y_1y_0			
		00	01	11	10
wy_2	00	d	0	0	d
	01	d	0	0	d
	11	d	1	1	d
	10	d	1	1	d

$$K_0 = w$$

		y_1y_0			
		00	01	11	10
wy_2	00	0	0	0	0
	01	d	d	d	d
	11	d	d	d	d
	10	0	0	1	0

$$J_2 = wy_0y_1$$

		y_1y_0			
		00	01	11	10
wy_2	00	0	0	d	d
	01	0	0	d	d
	11	0	1	d	d
	10	0	1	d	d

$$J_1 = wy_0$$


		y_1y_0			
		00	01	11	10
wy_2	00	d	d	0	0
	01	d	d	0	0
	11	d	d	1	0
	10	d	d	1	0

$$K_1 = wy_0$$

		y_1y_0			
		00	01	11	10
wy_2	00	d	d	d	d
	01	0	0	0	0
	11	0	0	1	0
	10	d	d	d	d

$$K_2 = wy_0y_1$$

Diagrama do circuito usando flip-flop JK

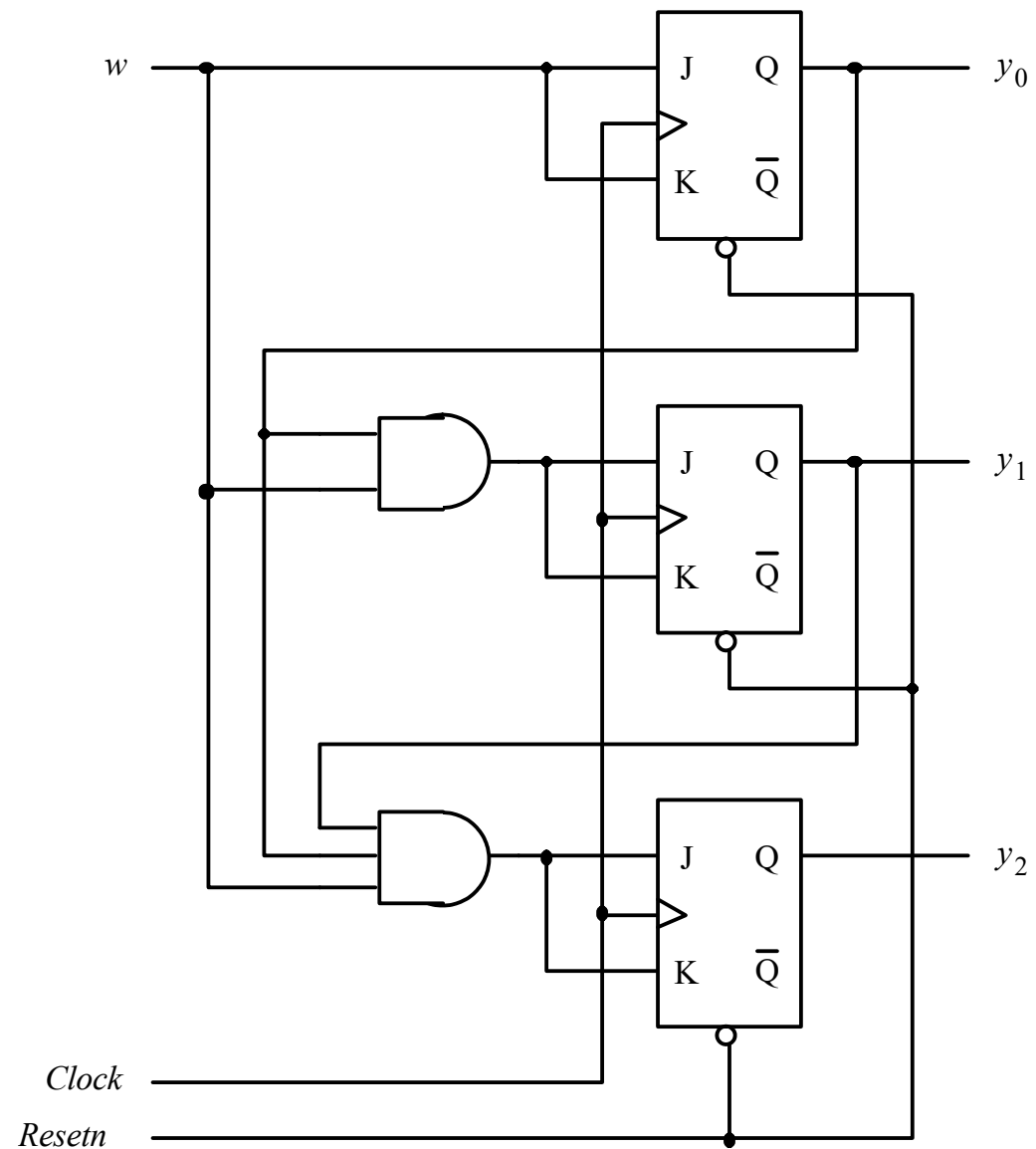

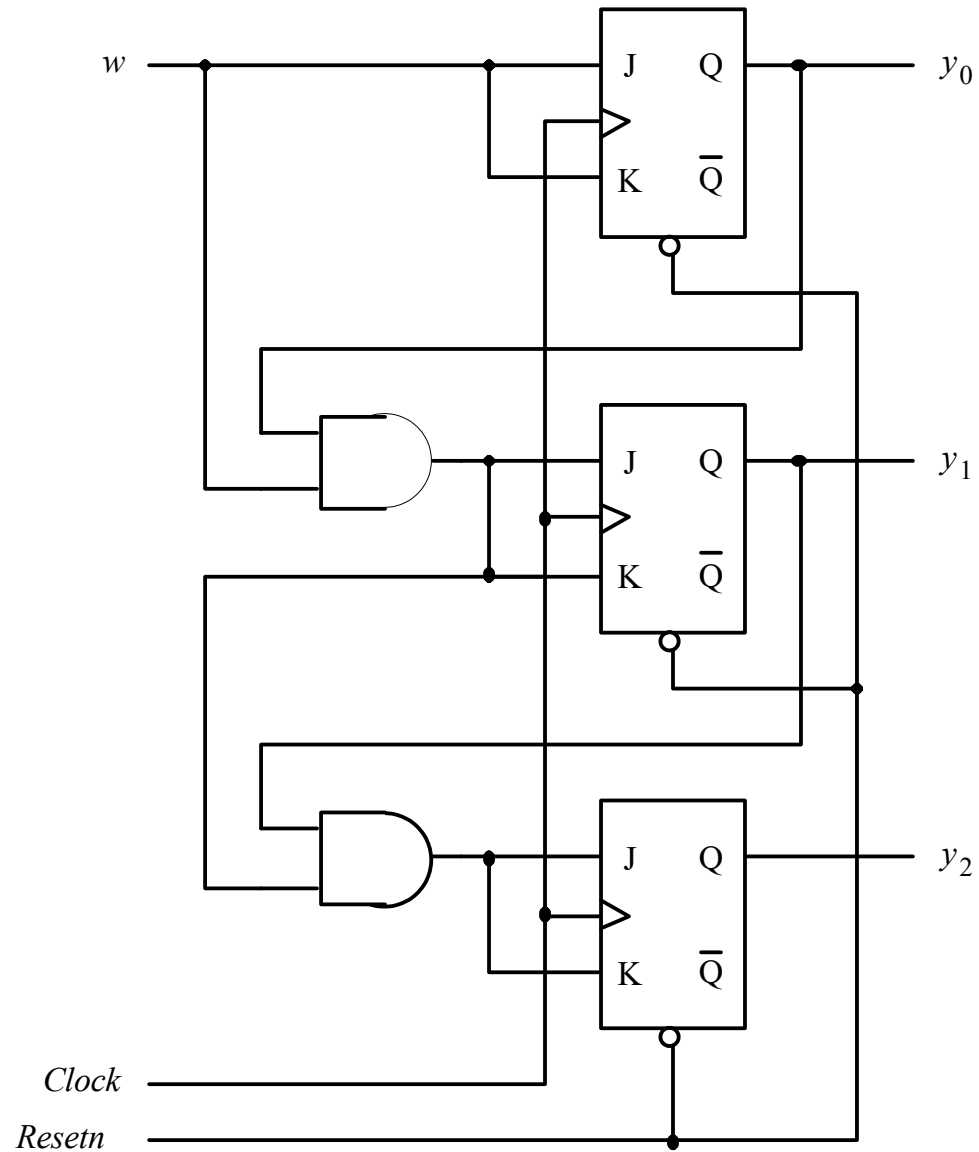


Figure 8.68 Factored-form implementation of the counter

Present state	Next state	Output $z_2z_1z_0$
A	B	000
B	C	100
C	D	010
D	E	110
E	F	001
F	G	101
G	H	011
H	A	111

Figure 8.69 State table for the counterlike example

Present state $y_2 y_1 y_0$	Next state $Y_2 Y_1 Y_0$	Output $z_2 z_1 z_0$
000	1 00	000
100	0 10	100
010	1 10	010
110	0 01	110
001	1 01	001
101	0 11	101
011	1 11	011
111	0 00	111

Figure 8.70 State-assigned table

 


Figure 8.71 Circuit for the counterlike example

Projete um circuito
que gerencie o acesso
a um recurso de um computador.
São 3 dispositivos, d1, d2 e d3,
sendo que d1 tem maior
prioridade que d2 e d3 e d2
tem maior prioridade que d3
MOORE

Entradas - requisições
r1r2r3

Saídas garantia de uso
g1g2g3

 


Figure 8.72 State diagram for the arbiter

 


Figure 8.73 Alternative style of state diagram for the arbiter

Projete um circuito
que gerencie o acesso
a um recurso de um computador.
São 3 dispositivos, d1, d2 e d3,
sendo que d1 tem maior
prioridade que d2 e d3 e d2
tem maior prioridade que d3
MEALY

Entradas - requisições

$r_1 r_2 r_3$

Saídas garantia de uso

$g_1 g_2 g_3$

 


Figure 8.73 Alternative style of state diagram for the arbiter

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY arbiter IS
    PORT (   Clock, Resetn   : IN        STD_LOGIC ;
            r                 : IN        STD_LOGIC_VECTOR(1 TO 3) ;
            g                 : OUT       STD_LOGIC_VECTOR(1 TO 3) ) ;
END arbiter ;

ARCHITECTURE Behavior OF arbiter IS
    TYPE State_type IS (Idle, gnt1, gnt2, gnt3) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN y <= Idle ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            CASE y IS
                WHEN Idle =>
                    IF r(1) = '1' THEN y <= gnt1 ;
                    ELSIF r(2) = '1' THEN y <= gnt2 ;
                    ELSIF r(3) = '1' THEN y <= gnt3 ;
                    ELSE y <= Idle ;
                    END IF ;
            ... con't

```

Figure 8.74a VHDL code for the arbiter

```

        WHEN gnt1 =>
            IF r(1) = '1' THEN y <= gnt1 ;
            ELSE y <= Idle ;
            END IF ;
        WHEN gnt2 =>
            IF r(2) = '1' THEN y <= gnt2 ;
            ELSE y <= Idle ;
            END IF ;
        WHEN gnt3 =>
            IF r(3) = '1' THEN y <= gnt3 ;
            ELSE y <= Idle ;
            END IF ;
    END CASE ;
END IF ;
END PROCESS ;
g(1) <= '1' WHEN y = gnt1 ELSE '0' ;
g(2) <= '1' WHEN y = gnt2 ELSE '0' ;
g(3) <= '1' WHEN y = gnt3 ELSE '0' ;
END Behavior ;

```

Figure 8.74b VHDL code for the arbiter (con't)

-
-
-

```
PROCESS( y )
BEGIN
    IF y = gnt1 THEN g(1) <= '1' ;
    ELSIF y = gnt2 THEN g(2) <= '1' ;
    ELSIF y = gnt3 THEN g(3) <= '1' ;
    END IF ;
END PROCESS ;
END Behavior ;
```

Figure 8.75 Incorrect VHDL code for the grant signals

```

•
•
•
PROCESS( y )
BEGIN
    g(1) <= '0' ;
    g(2) <= '0' ;
    g(3) <= '0' ;
    IF y = gnt1 THEN g(1) <= '1' ;
    ELSIF y = gnt2 THEN g(2) <= '1' ;
    ELSIF y = gnt3 THEN g(3) <= '1' ;
    END IF ;
END PROCESS ;
END Behavior ;

```

Figure 8.76 Correct VHDL code for the grant signals



 


Figure 8.77 Simulation results for the arbiter circuit

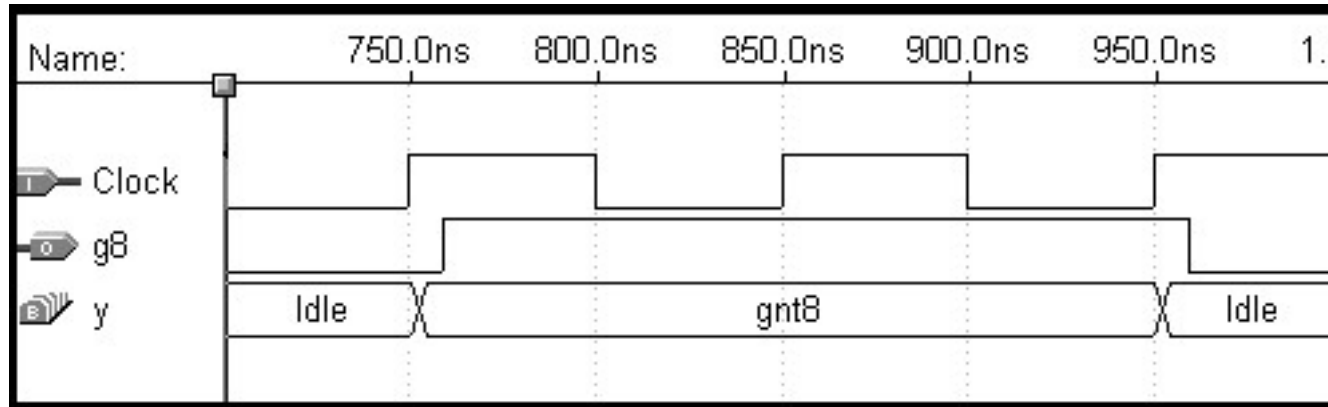

a) Output delays using binary encoding

 

b) Output delays using one-hot encoding

Figure 8.78 Output delays in the arbiter circuit

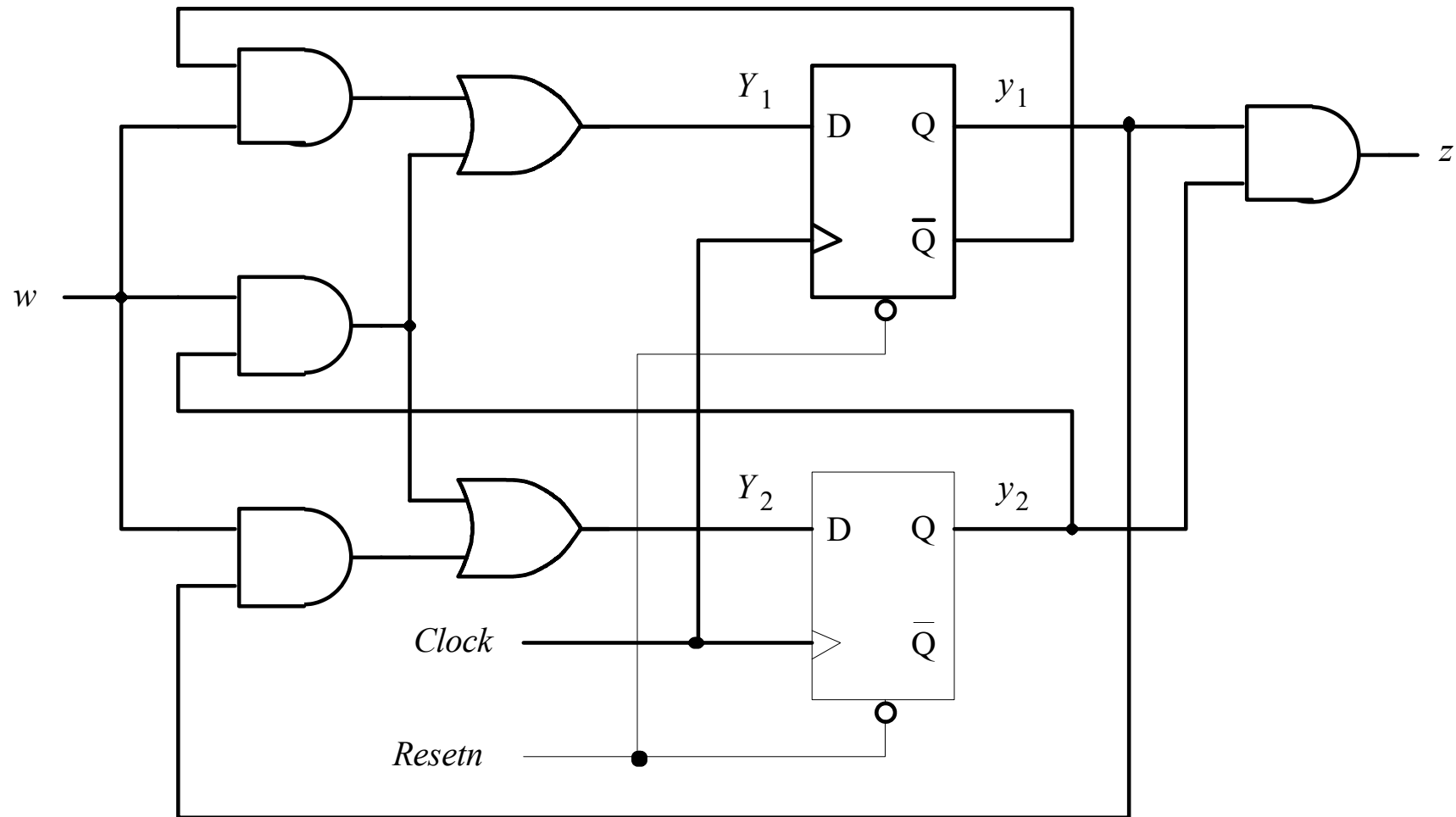


Figure 8.80 Circuit for Example 8.8

Present state y_2y_1	Next State		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
0 0	0 0	01	0
0 1	0 0	10	0
1 0	0 0	11	0
1 1	0 0	11	1

(a) State-assigned table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

(b) State table

Figure 8.81 Tables for the circuit in Example 8.8

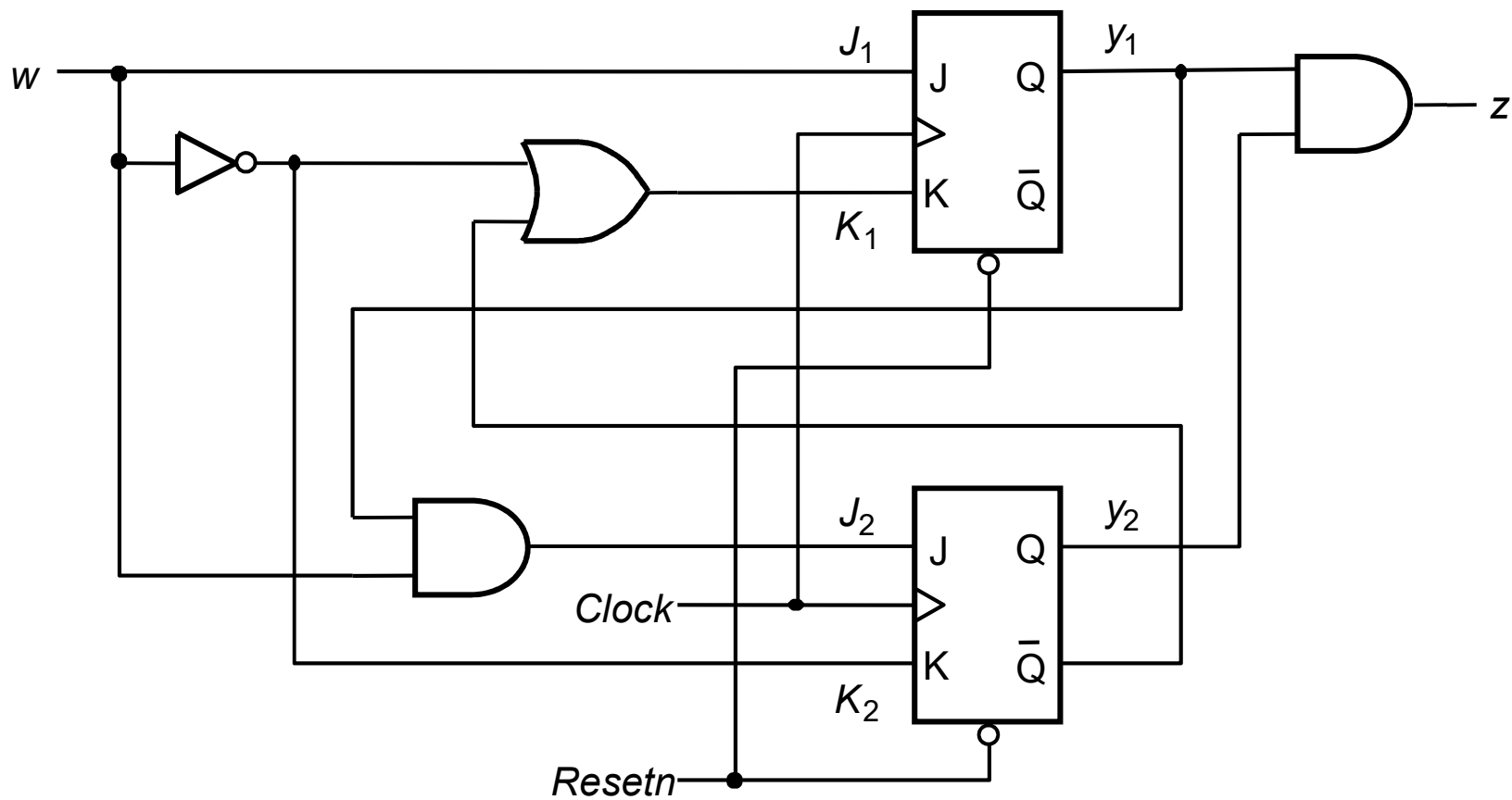


Figure 8.82 Circuit for Example 8.9

Present state y_2y_1	Flip-flop inputs				Output z
	$w = 0$		$w = 1$		
	J_2K_2	J_1K_1	J_2K_2	J_1K_1	
00	01	0 1	0 0	1 1	0
01	01	0 1	1 0	1 1	0
10	01	0 1	0 0	1 0	0
11	01	0 1	1 0	1 0	1

Figure 8.83 Excitation table


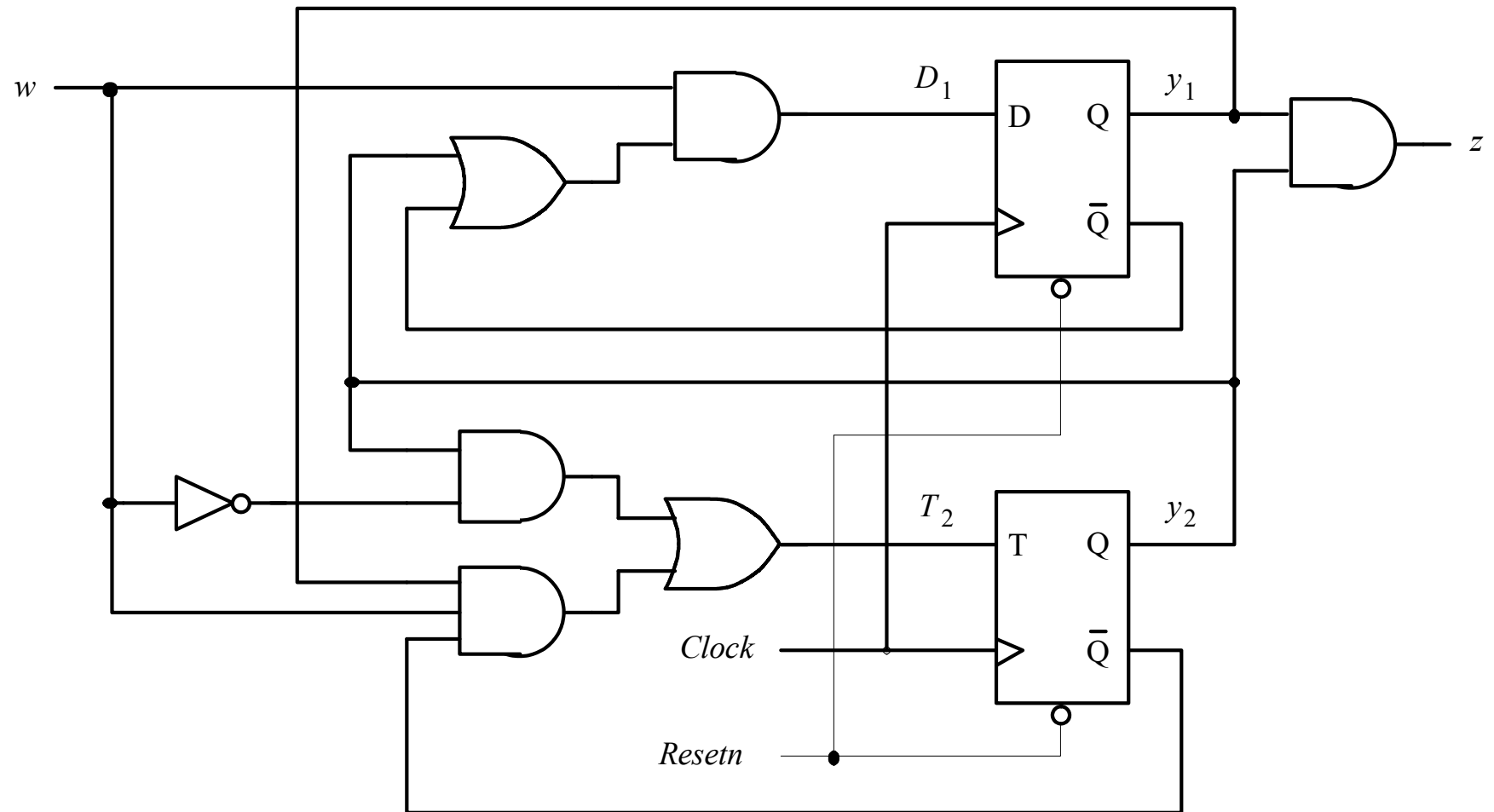



Figure 8.84 Circuit for Example 8.10

Present state y_2y_1	Flip-flop inputs		Output z
	$w = 0$	$w = 1$	
	T_2D_1	T_2D_1	
0 0	0 0	01	0
0 1	0 0	10	0
1 0	1 0	01	0
1 1	1 0	01	1


Figure 8.85 Excitation table

 

(a) State box

 

(b) Decision box

 

(c) Conditional output box

Figure 8.86 Elements used in ASM charts

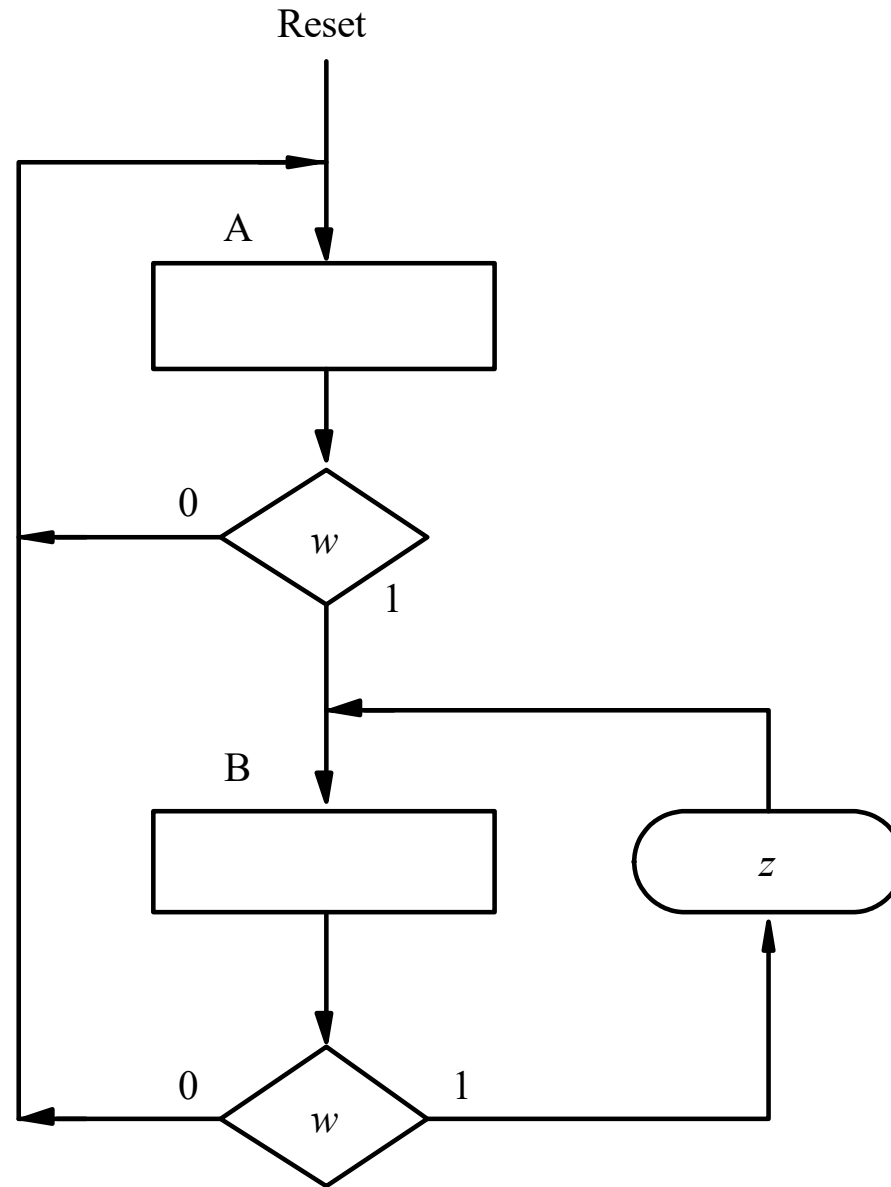


Figure 8.88 ASM chart for the FSM in Figure 8.23

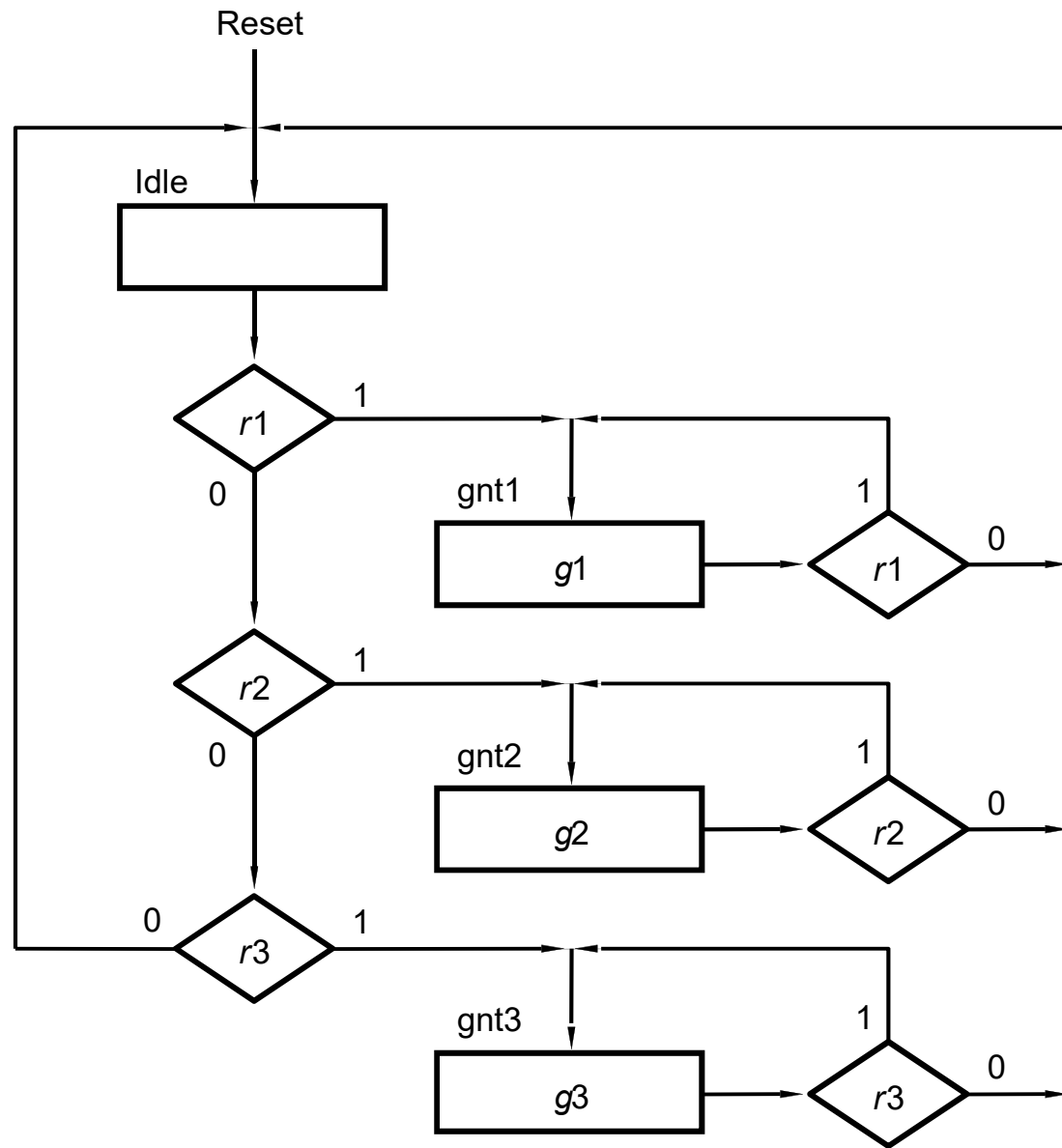


Figure 8.89 ASM chart for the arbiter

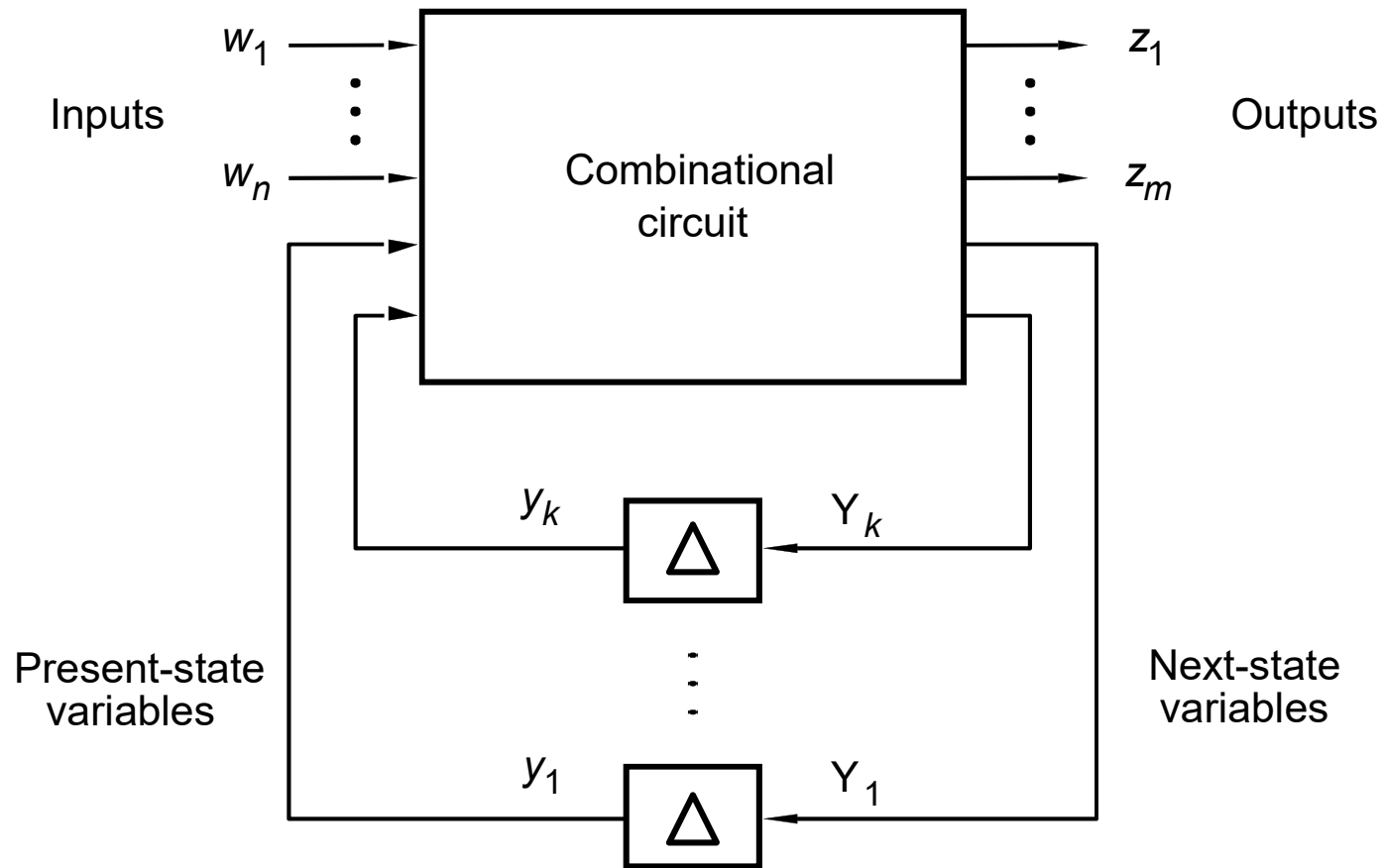


Figure 8.90 The general model for a sequential circuit

Present state y_2y_1	Next state		Output z
	$w = 0$	$w = 1$	
	Y_2Y_1	Y_2Y_1	
0 0	1 0	1 1	0
0 1	0 1	0 0	0
1 0	1 1	0 0	0
1 1	1 0	0 1	1

Figure P8.1 State-assigned table for problems 8.1 and 8.2

 


Figure P8.2 Circuit for problem 8.29

