

Circuitos Lógicos e Organização de Computadores

Capítulo 6 – Blocos com Circuitos Combinacionais


Ricardo Pannain

pannain@unicamp.br

Blocos Básicos com Circuitos Combinacionais

- **Projetar:**
 - Multiplexador 2-para-1
 - Multiplexador 4-para-1
 - Multiplexador 4-para-1 construído a partir de multiplexadores 2-para-1
 - Multiplexador 16-para-1 construído a partir de multiplexadores 4-para-1


Multiplexador 2-para-1

 


(a) Símbolo Gráfico

s	f
0	w_0
1	w_1

(b) Tabela Verdade

 


(c) Circuito SOP

 

(d) Circuito com Transmission Gate 3


Multiplexador 4-para-1

 

(a) Símbolo Gráfico


s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Tabela Verdade

 

 (c) Circuito


Multiplexador 4-para-1 construído a partir de multiplexadores 2-para-1




s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

 (b) Tabela Verdade

Multiplexador 16-para-1 construído a partir de multiplexadores 4-para-1




Aplicação prática de multiplexadores

 


(a) Uma chave crossbar 2x2

Aplicação prática de multiplexadores

 


(a) Uma chave crossbar 2x2

 


 (b) Implementação com multiplexadores

Síntese de uma função lógica usando multiplexadores



 (a) Implementação usando um multiplexador 4-para-1



(b) Tabela verdade modificada

(c) Circuito

Síntese de uma função lógica de 3 entradas usando multiplexadores


w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(a) Tabela verdade modificada

Síntese de uma função lógica de 3 entradas usando multiplexadores

w_1	w_2	w_3	f		w_1	w_2	f
0	0	0	0	}	0	0	0
0	0	1	0		0	1	w_3
0	1	0	0		1	0	w_3
0	1	1	1		1	1	1
1	0	0	0	}			
1	0	1	1				
1	1	0	1	}			
1	1	1	1				

(a) Tabela verdade modificada

 

(b) Circuito

Função XOR de 3 entradas

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


(a) Tabela Verdade

Função XOR de 3 entradas

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$w_2 \oplus w_3$

$\overline{w_2 \oplus w_3}$

 

(a) Tabela Verdade

(b) Circuito


$$x = w$$

$$f = x_1'(x_2'x_3 + x_2x_3') + x_1(x_2x_3 + x_2'x_3') = x_1 \text{ XOR } x_2 \text{ XOR } x_3 = (x_1 \text{ XOR } x_2) \text{ XOR } x_3$$

Função XOR de 3 entradas

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Tabela Verdade

 

(b) Circuito

Teorema de Shannon

$$f(w_1, w_2, \dots, w_n) = \overline{w_1} \cdot f(0, w_2, \dots, w_n) + w_1 \cdot \underbrace{f(1, w_2, \dots, w_n)}_{\text{co-fator}}$$

$$f(w_1, w_2, \dots, w_n) = \overline{w_i} f_{\overline{w_i}} + w_i f_{w_i}$$

Exercícios:

1) $f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$

2) Para xor de 3 entradas: $f = w_1 \text{ xor } (w_2 \text{ xor } w_3)$

3) $f = w_1' w_3' + w_1 w_2 + w_1 w_3$

Síntese de uma função lógica de 3 entradas usando multiplexadores

Exercícios:

1)

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$f = w_1' (w_2 w_3) + w_1 (w_2 + w_3)$$


Obs:

$$\begin{aligned} f w_1 &= w_2 + w_3 + w_2 w_3 = w_2 (1 + w_3) + w_3 (1 + w_2) = \\ &= w_2 + w_3 \end{aligned}$$

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

(b) Tabela Verdade

 

(b) Circuito

$$1) \quad f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$f w_1' = w_2 w_3$$

$$f w_1 = w_2 + w_3 + w_2 w_3 = w_2 + w_3$$

$$f = w_1' (w_2 w_3) + w_1 (w_2 + w_3)$$

$$f w_1' w_2' = 0$$

$$f w_1' w_2 = w_3$$

$$f w_1 w_2' = w_3$$

$$f w_1 w_2 = 1$$

Exercícios:

w_1	w_2	w_3	f		w_1	f
0	0	0	0	}	0	$w_2 w_3$
0	0	1	0			
0	1	0	0			
0	1	1	1			
1	0	0	0	}	1	$w_2 + w_3$
1	0	1	1			
1	1	0	1			
1	1	1	1			

1) $f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$

Exercícios:

$$1) \quad f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$f w_1' = w_2 w_3$$

$$f w_1 = w_2 + w_3 + w_2 w_3 = w_2 + w_3$$

$$f = w_1' (w_2 w_3) + w_1 (w_2 + w_3)$$

$$f w_1' w_2' = 0$$

$$f w_1' w_2 = w_3$$

$$f w_1 w_2' = w_3$$

$$f w_1 w_2 = 1$$

$$f w_1' w_2' w_3' = 0$$

$$f w_1' w_2' w_3 = 0$$

$$f w_1' w_2 w_3' = 0$$

$$f w_1' w_2 w_3 = 1$$

$$f w_1 w_2' w_3' = 0$$

$$f w_1 w_2' w_3 = 1$$


$$f w_1 w_2 w_3' = 1$$

$$f w_1 w_2 w_3 = 1$$

Exercícios:

w_1	w_2	w_3	f		w_1	f
0	0	0	0	}	0	$w_2 w_3$
0	0	1	0			$w_2 + w_3$
0	1	0	0		}	
0	1	1	1			
1	0	0	0			
1	0	1	1			
1	1	0	1			
1	1	1	1			

 Exemplos de circuitos com multiplexadores



2) *Para xor de 3 entradas:*

$$f = w1 \text{ xor } (w2 \text{ xor } w3)$$
$$f = w1' (w2 \text{ xor } w3) + w1 \overline{(w2 \text{ xor } w3)}$$

$$f = w1' (w2'w3 + w2w3') + w1 (w2'w3' + w2w3)$$

$$f = w1'w2'(g) + w1'w2(h) + w1w2'(i) + w1w2(j)$$

$$g = w3 = fw1'w2'$$

$$h = w3' = fw1'w2$$

$$i = w3' = fw1w2'$$

$$j = w3 = fw1w2$$

$$3) \quad f = w_1'w_3' + w_1w_2 + w_1w_3$$

Em função de w_1

$$f_{w_1'} = w_3'$$

$$f_{w_1} = w_2 + w_3$$

Em função de w_1 e w_2

$$f_{w_1', w_2'} = w_3'$$

$$f_{w_1', w_2} = w_3'$$

$$f_{w_1w_2'} = w_3$$

$$f_{w_1w_2} = 1$$

Em função de w_1 e w_2 e w_3

$$f_{w_1', w_2', w_3'} = 1$$

$$f_{w_1', w_2', w_3} = 0$$

$$f_{w_1', w_2w_3'} = 1$$

$$f_{w_1', w_2w_3} = 0$$


$$f_{w_1w_2', w_3'} = 0$$

$$f_{w_1w_2', w_3} = 1$$


$$f_{w_1w_2w_3'} = 1$$

$$f_{w_1w_2w_3} = 1$$

 Exemplos de circuitos com multiplexadores



(a) Using a 2-to-1 multiplexer

 

(b) Using a 4-to-1 multiplexer

Exemplo

Em função de w_1 e w_2

$$f = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$f_{w_1} = w_2 w_3$$

$$f_{w_1} = w_2 + w_3$$

$$\begin{aligned} \text{OBS: } w_2 + w_3 + w_2 w_3 &= w_2(1 + w_3) + \\ &+ w_3(1 + w_2) = w_2 + w_3 \end{aligned}$$

$$f_{w_1, w_2} = 0$$

$$f_{w_1, w_2} = w_3$$


$$f_{w_1 w_2} = w_3$$

$$f_{w_1 w_2} = 1$$

Decodificador n -para- 2^n

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Tabela Verdade

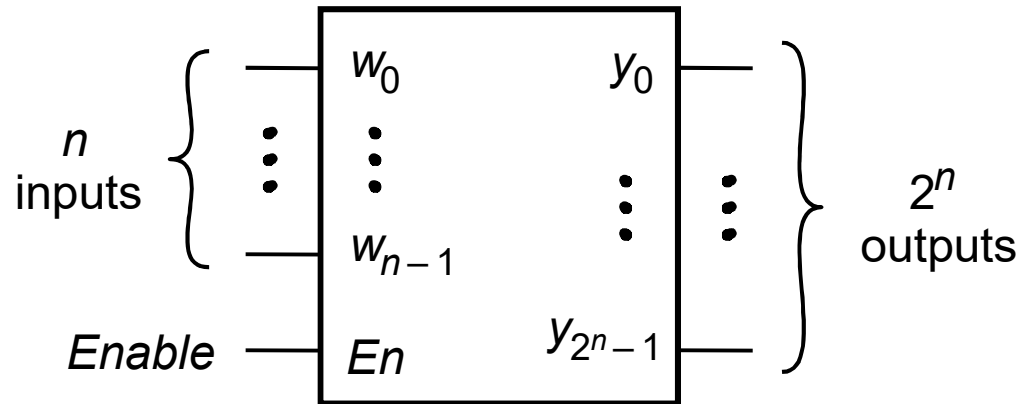


Se $Enable = 0 \rightarrow y_i = 0$; para qualquer $w_1 w_0$

Se $Enable = 1 \rightarrow w_1 w_0 = 00 \rightarrow \text{só } y_0 = 1$; $01 \rightarrow \text{só } y_1 = 1$;
 $w_1 w_0 = 10 \rightarrow \text{só } y_2 = 1$ e $11 \rightarrow \text{só } y_3 = 1$


Decodificador 2-para-4

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Tabela Verdade

 

(b) Símbolo Gráfico

 

(c) Circuito Lógico


1-Decodificador 3 para 8, utilizando decodificadores 2 para 4

w2

0 decod 1 - entradas w1 w0

1 decod 2 - entradas w1 w0

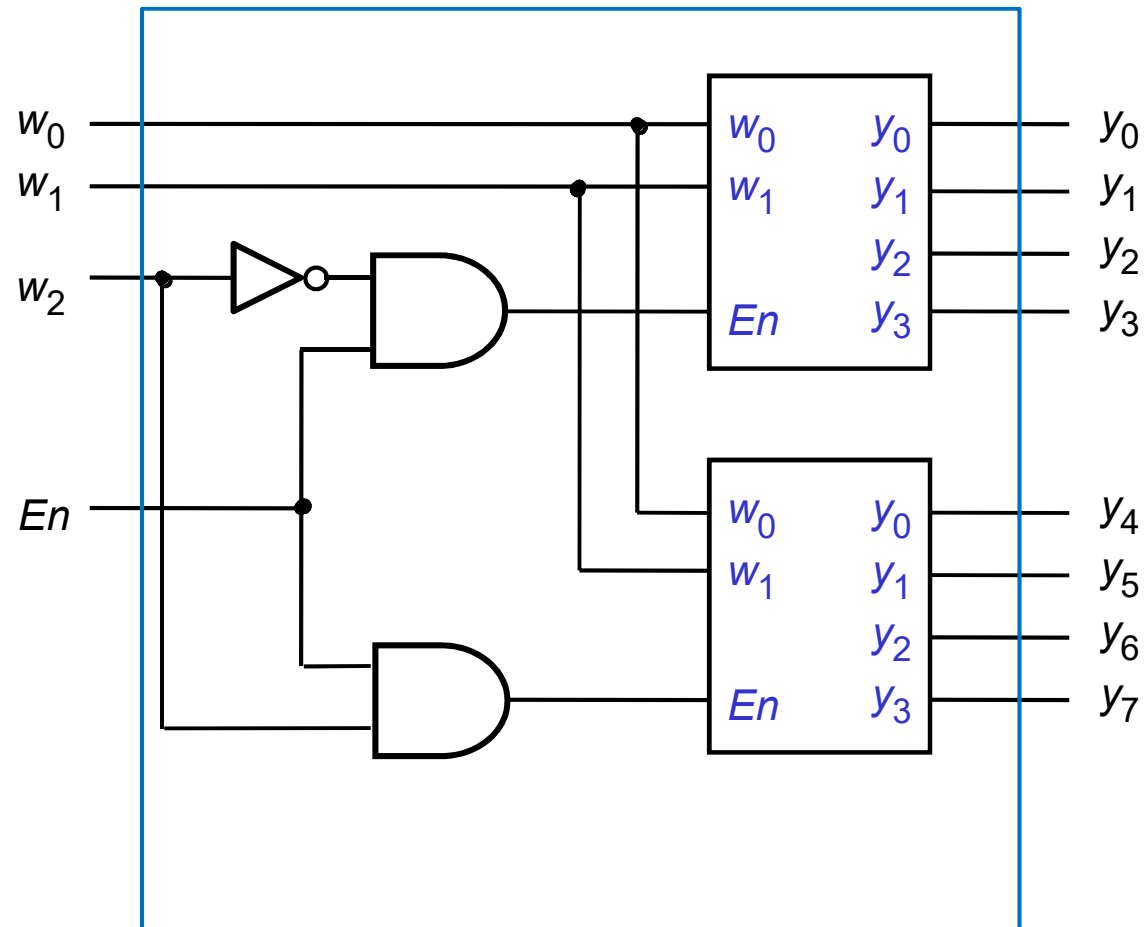Decodificador 3-para-8 usando dois decodificadores 2-para-4



2 – Decodificador 4 para 16, com decodificadores 2 para 4

w3 w2


0 0 decod1 - entradas w1 w0

0 1 decod2 - entradas w1 w0

1 0 decod3 - entradas w1 w0


1 1 decod4 - entradas w1 w0

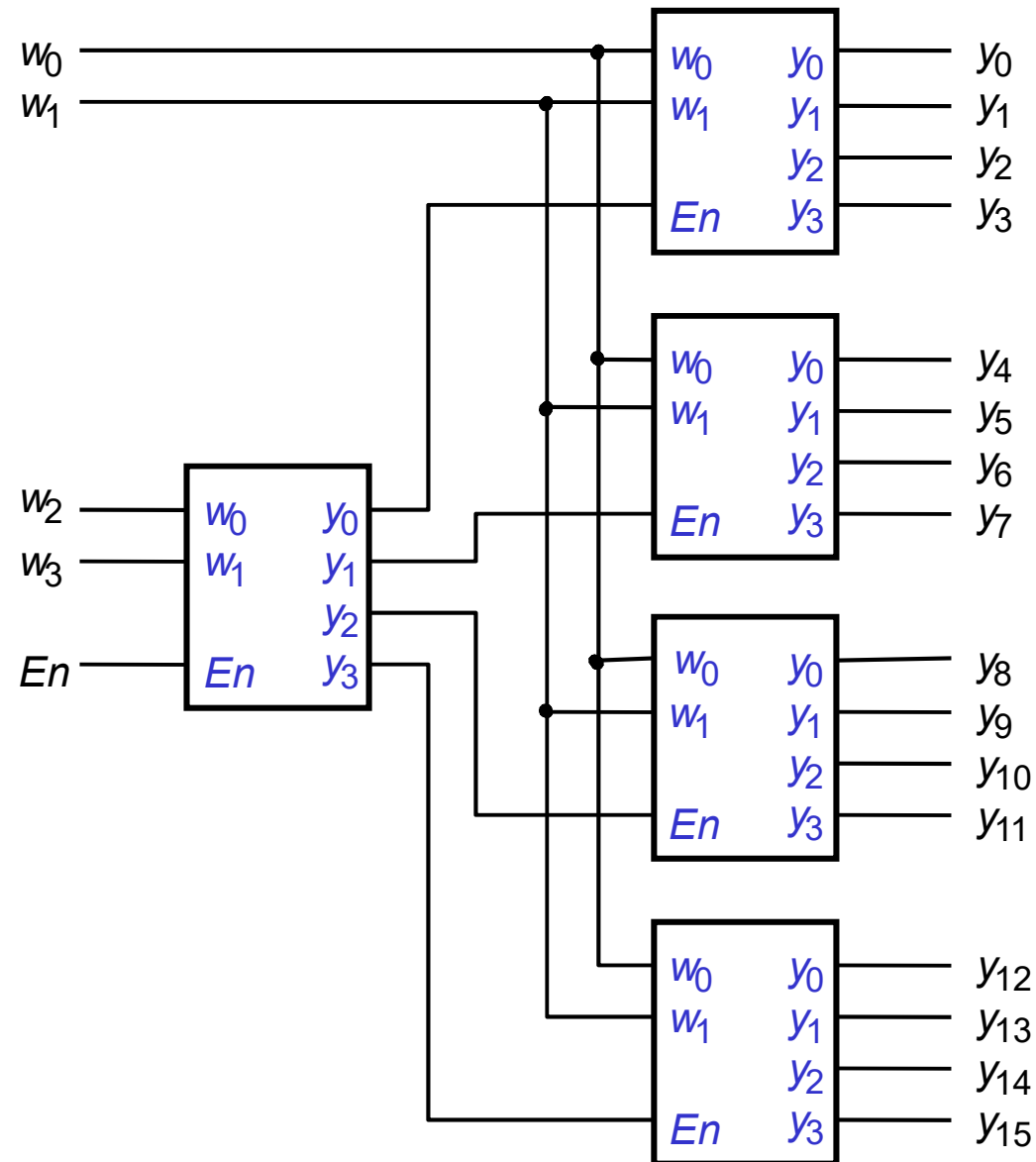Decodificador 4-to-16 usando decodificadores 2-para-4




3 – MUX 4:1 com decodificador (2:4)

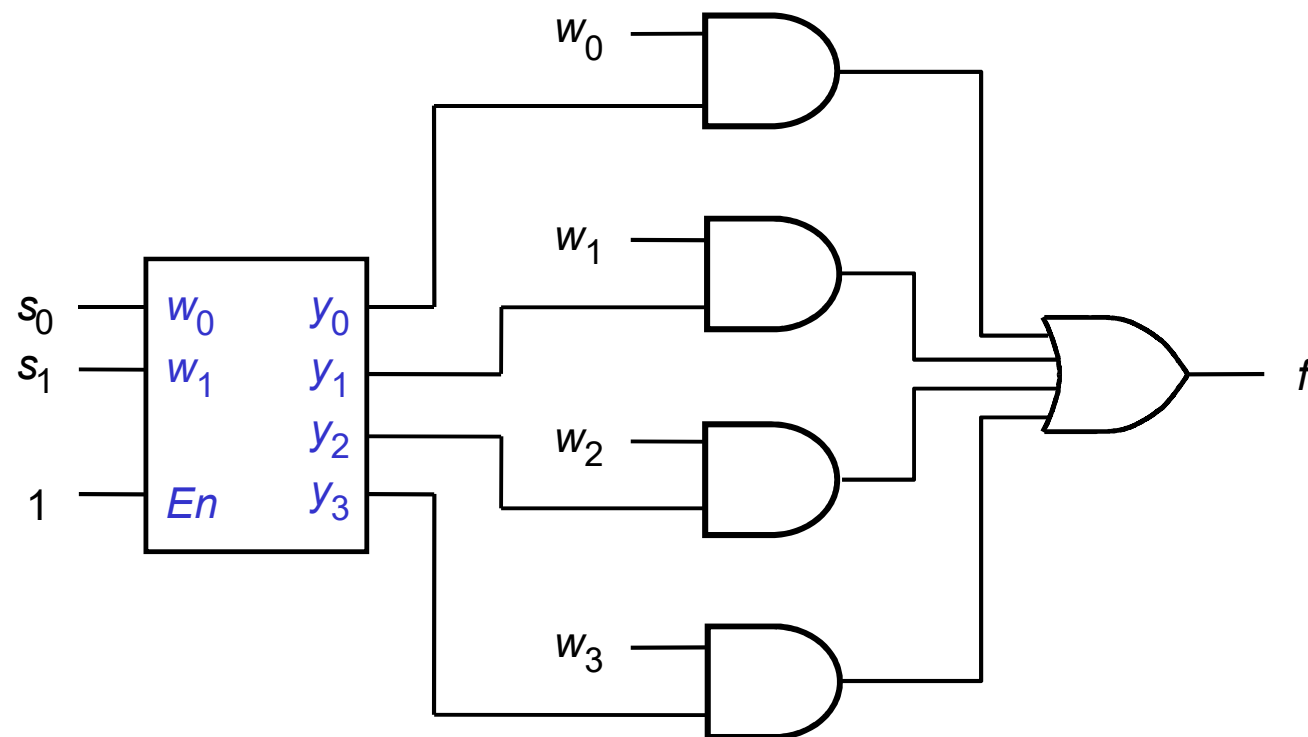
Multiplexador 4-para-1 usando um decodificador



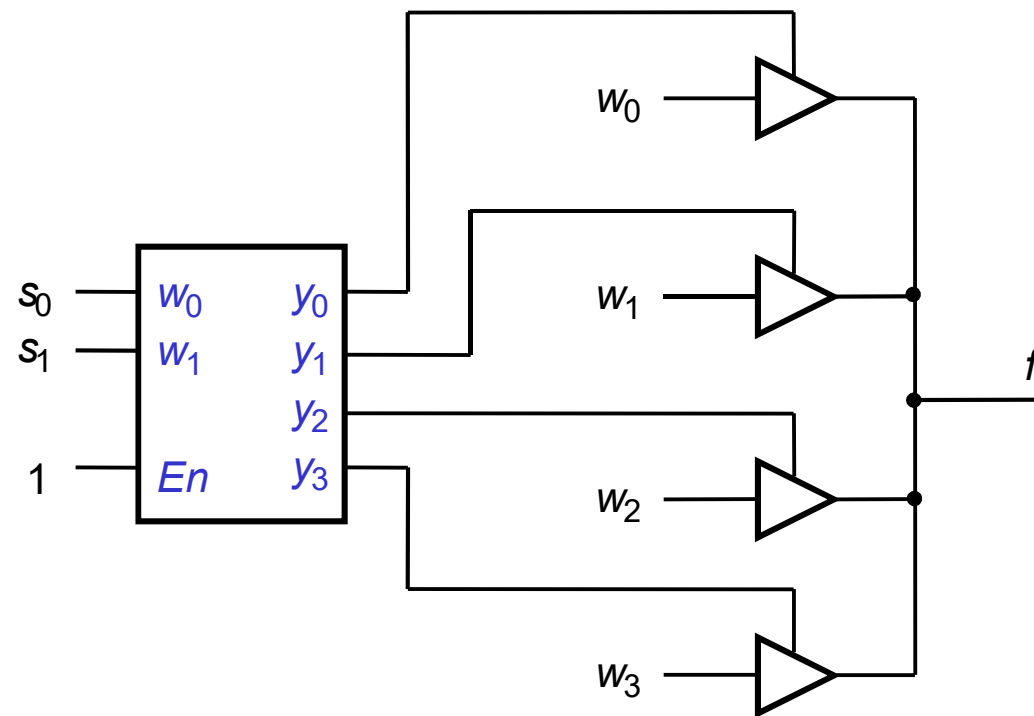
Multiplexador 4-para-1 usando um decodificador e buffers tri-state



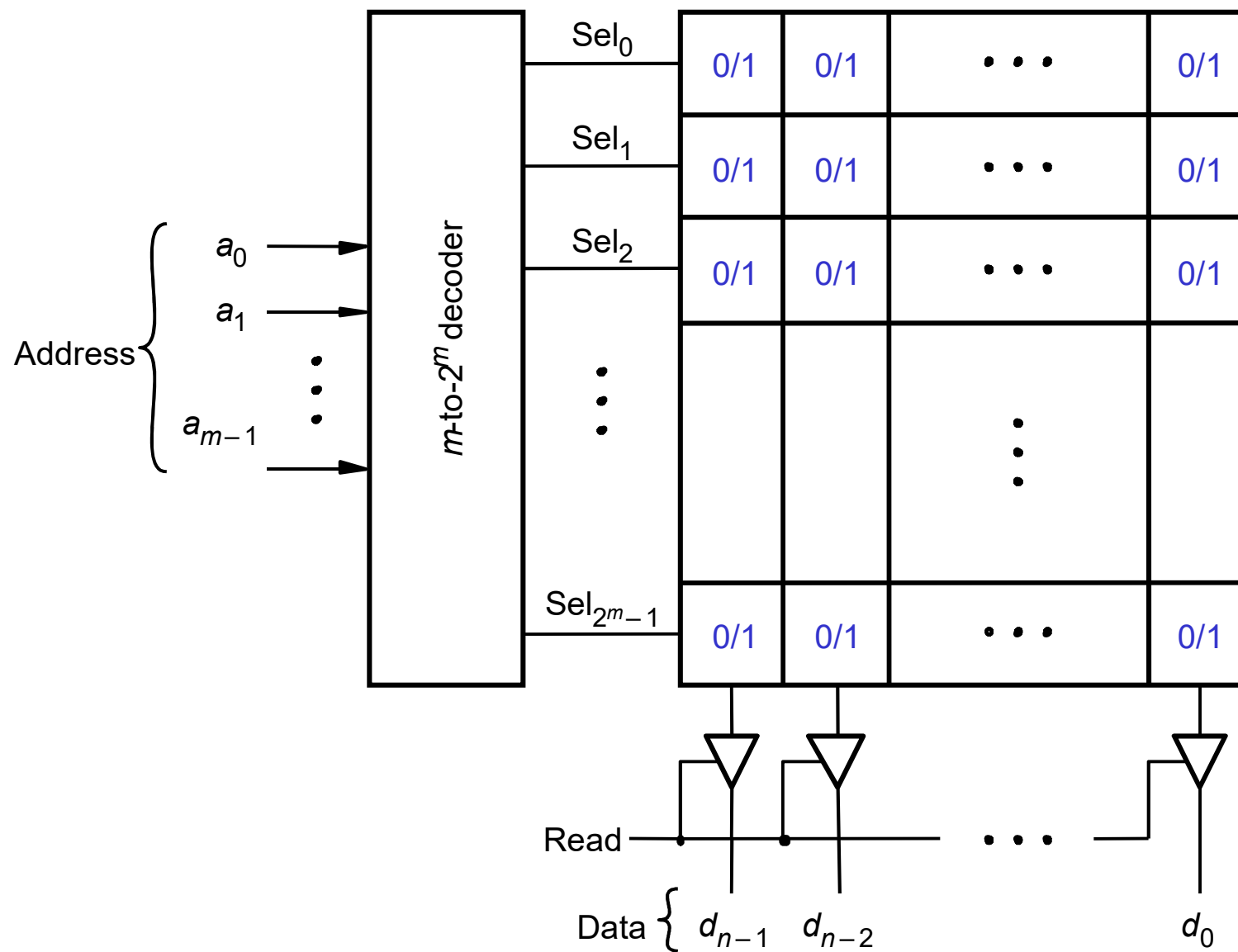Bloco de memória *read only* (ROM) $2^m \times n$



Codificador binário 2^n -para- n

 


Que gere o par y_1y_0 , que identifique qual de 4 entradas (w_0, w_1, w_2, w_3) está ativa, ou seja,
00 se $w_0 = 1$ e restante = 0, 01 se $w_1 = 1$ e restante = 0,
10 se $w_2 = 1$ e restante = 0,
11 se $w_3 = 1$ e restante = 0,

Codificador binário 4-para-2

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Tabela Verdade

w3	w2	w1	w0	y1	y0
0	0	0	0	d	d
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	d	d
0	1	0	0	1	0
0	1	0	1	d	d
0	1	1	0	d	d
0	1	1	1	d	d
1	0	0	0	1	1
1	0	0	1	d	d
1	0	1	0	d	d
1	0	1	1	d	d
1	1	0	0	d	d
1	1	0	1	d	d
1	1	1	0	d	d
1	1	1	1	d	d

 

(b) Circuito

Tabela Verdade para um codificador de prioridade 4-para-2

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

Tabela Verdade para um codificador de prioridade 4-para-2

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$z = w_3 + w_2 + w_1 + w_0$$

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0	d	d
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1


	00	01	11	10
00	d	1	1	1
01	0	1	1	1
11	0	1	1	1
10	0	1	1	1

$$y_1 = w_2 + w_3$$


	00	01	11	10
00	d	0	1	1
01	0	0	1	1
11	1	0	1	1
10	1	0	1	1

$$y_0 = w_3 + w_2'w_1$$

 Conversor BCD para display de 7 segmentos



(a) Code converter

 


(b) 7-segment display

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

(c) Truth table

Exercício – projetar um comparador de 2 números de 4 bits (AeqB, AgtB, AltB)

Circuito Comparador de quatro bits

 

Código VHDL para um multiplexador 2-para-1

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN '0',
           w1 WHEN OTHERS ;
END Behavior ;
```

Código VHDL para um multiplexador 4-para-1

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT ( w0, w1, w2, w3    : IN      STD_LOGIC ;
           s                  : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           f                  : OUT     STD_LOGIC ) ;
END mux4to1 ;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN "00",
            w1 WHEN "01",
            w2 WHEN "10",
            w3 WHEN OTHERS ;
END Behavior ;
```

Declaração de componente para multiplexador 4-para-1

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
PACKAGE mux4to1_package IS
    COMPONENT mux4to1
        PORT ( w0, w1, w2, w3 : IN      STD_LOGIC ;
              s               : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
              f               : OUT      STD_LOGIC ) ;
    END COMPONENT ;
END mux4to1_package ;
```

Código hierárquico para multiplexador 16-para-1

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
LIBRARY work ;
USE work.mux4to1_package.all ;

ENTITY mux16to1 IS
    PORT ( w   : IN      STD_LOGIC_VECTOR(0 TO 15) ;
           s   : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           f   : OUT     STD_LOGIC ) ;
END mux16to1 ;

ARCHITECTURE Structure OF mux16to1 IS
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
BEGIN
    Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3), s(1 DOWNT0 0), m(0) ) ;
    Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7), s(1 DOWNT0 0), m(1) ) ;
    Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11), s(1 DOWNT0 0), m(2) ) ;
    Mux4: mux4to1 PORT MAP ( w(12), w(13), w(14), w(15), s(1 DOWNT0 0), m(3) ) ;
    Mux5: mux4to1 PORT MAP
        ( m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f ) ;
END Structure ;
```

Código VHDL para um decodificador binário 2-para-4

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w   : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           En  : IN      STD_LOGIC ;
           y   : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;

ARCHITECTURE Behavior OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "1000" WHEN "100",
            "0100" WHEN "101",
            "0010" WHEN "110",
            "0001" WHEN "111",
            "0000" WHEN OTHERS ;
END Behavior ;
```

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    f <= w0 WHEN s = '0' ELSE w1 ;
END Behavior ;

```

Figure 6.31 A 2-to-1 multiplexer using a conditional signal assignment


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w   : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
           y   : OUT     STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           z   : OUT     STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    y <=  "11" WHEN w(3) = '1' ELSE
          "10" WHEN w(2) = '1' ELSE
          "01" WHEN w(1) = '1' ELSE
          "00" ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;

```

Figure 6.32 VHDL code for a priority encoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT     STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT     STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    WITH w SELECT
        y <=  "00" WHEN "0001",
              "01" WHEN "0010",
              "01" WHEN "0011",
              "10" WHEN "0100",
              "10" WHEN "0101",
              "10" WHEN "0110",
              "10" WHEN "0111",
              "11" WHEN OTHERS ;
    WITH w SELECT
        z <=  '0' WHEN "0000",
              '1' WHEN OTHERS ;
END Behavior ;

```

Figure 6.33 Less efficient code for a priority encoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY compare IS
    PORT ( A, B          : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           AeqB, AgtB, AltB : OUT   STD_LOGIC ) ;
END compare ;

ARCHITECTURE Behavior OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END Behavior ;

```

Figure 6.34 VHDL code for a four-bit comparator

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_arith.all ;

ENTITY compare IS
    PORT ( A, B          : IN      SIGNED(3 DOWNT0 0) ;
           AeqB, AgtB, AltB : OUT   STD_LOGIC ) ;
END compare ;

ARCHITECTURE Behavior OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END Behavior ;

```

Figure 6.35 A four-bit comparator using signed numbers

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.mux4to1_package.all ;

ENTITY mux16to1 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(0 TO 15) ;
           s      : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           f      : OUT     STD_LOGIC ) ;
END mux16to1 ;

ARCHITECTURE Structure OF mux16to1 IS
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
BEGIN
    G1: FOR i IN 0 TO 3 GENERATE
        Muxes: mux4to1 PORT MAP (
            w(4*i), w(4*i+1), w(4*i+2), w(4*i+3), s(1 DOWNT0 0), m(i) ) ;
    END GENERATE ;
    Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNT0 2), f ) ;
END Structure ;

```

Figure 6.36 Code for a 16-to-1 multiplexer using a generate statement

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec4to16 IS
    PORT (
        w      : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
        En     : IN      STD_LOGIC ;
        y      : OUT     STD_LOGIC_VECTOR(0 TO 15) ) ;
END dec4to16 ;

ARCHITECTURE Structure OF dec4to16 IS
    COMPONENT dec2to4
        PORT (
            w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
            En     : IN      STD_LOGIC ;
            y      : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
    END COMPONENT ;
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
BEGIN
    G1: FOR i IN 0 TO 3 GENERATE
        Dec_ri: dec2to4 PORT MAP ( w(1 DOWNTO 0), m(i), y(4*i TO 4*i+3) );
        G2: IF i=3 GENERATE
            Dec_left: dec2to4 PORT MAP ( w(i DOWNTO i-1), En, m ) ;
        END GENERATE ;
    END GENERATE ;
END Structure ;

```

Figure 6.37 Hierarchical code for a 4-to-16 binary decoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        IF s = '0' THEN
            f <= w0 ;
        ELSE
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

Figure 6.38 A 2-to-1 multiplexer specified using an if-then-else statement 55

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s      : IN      STD_LOGIC ;
           f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        f <= w0 ;
        IF s = '1' THEN
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

Figure 6.39 Alternative code for a 2-to-1 multiplexer


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY priority IS
    PORT (
        w    : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
        y    : OUT    STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        z    : OUT    STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    PROCESS ( w )
    BEGIN
        IF w(3) = '1' THEN
            y <= "11" ;
        ELSIF w(2) = '1' THEN
            y <= "10" ;
        ELSIF w(1) = '1' THEN
            y <= "01" ;
        ELSE
            y <= "00" ;
        END IF ;
    END PROCESS ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;

```

Figure 6.40 A priority encoder specified using if-then-else

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT (
        w : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT     STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT     STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    PROCESS ( w )
    BEGIN
        y <= "00" ;
        IF w(1) = '1' THEN y <= "01" ; END IF ;
        IF w(2) = '1' THEN y <= "10" ; END IF ;
        IF w(3) = '1' THEN y <= "11" ; END IF ;

        z <= '1' ;
        IF w = "0000" THEN z <= '0' ; END IF ;
    END PROCESS ;
END Behavior ;

```

Figure 6.41 Alternative code for the priority encoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY compare1 IS
    PORT (  A, B      : IN      STD_LOGIC ;
           AeqB      : OUT     STD_LOGIC ) ;
END compare1 ;

ARCHITECTURE Behavior OF compare1 IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        AeqB <= '0' ;
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

Figure 6.42 Code for a one-bit equality comparator

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY implied IS
    PORT ( A, B      : IN      STD_LOGIC ;
           AeqB      : OUT     STD_LOGIC ) ;
END implied ;

ARCHITECTURE Behavior OF implied IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

Figure 6.43 An example of code that results in implied memory

```

...
PROCESS ( A, B )
BEGIN
    IF A = B THEN
        AeqB <= '1' ;
    END IF ;
END PROCESS ;
...

```

 


Figure 6.44 Circuit generated due to implied memory

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN  STD_LOGIC ;
           f          : OUT STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        CASE s IS
            WHEN '0' =>
                f <= w0 ;
            WHEN OTHERS =>
                f <= w1 ;
        END CASE ;
    END PROCESS ;
END Behavior ;

```

Figure 6.45 A CASE statement that represents a 2-to-1 multiplexer

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           En      : IN      STD_LOGIC ;
           y       : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;

ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
    PROCESS ( w, En )
    BEGIN
        IF En = '1' THEN
            CASE w IS
                WHEN "00" =>      y <= "1000" ;
                WHEN "01" =>      y <= "0100" ;
                WHEN "10" =>      y <= "0010" ;
                WHEN OTHERS =>    y <= "0001" ;
            END CASE ;
        ELSE
            y <= "0000" ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

Figure 6.46 A 2-to-4 binary decoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY seg7 IS
    PORT (    bcd    : IN        STD_LOGIC_VECTOR(3 DOWNT0 0) ;
            leds    : OUT        STD_LOGIC_VECTOR(1 TO 7) ) ;
END seg7 ;
ARCHITECTURE Behavior OF seg7 IS
BEGIN
    PROCESS ( bcd )
    BEGIN
        CASE bcd IS
            --          abcdefg
            WHEN "0000" => leds <= "1111110" ;
            WHEN "0001" => leds <= "0110000" ;
            WHEN "0010" => leds <= "1101101" ;
            WHEN "0011" => leds <= "1111001" ;
            WHEN "0100" => leds <= "0110011" ;
            WHEN "0101" => leds <= "1011011" ;
            WHEN "0110" => leds <= "1011111" ;
            WHEN "0111" => leds <= "1110000" ;
            WHEN "1000" => leds <= "1111111" ;
            WHEN "1001" => leds <= "1110011" ;
            WHEN OTHERS => leds <= "-----" ;
        END CASE ;
    END PROCESS ;
END Behavior ;

```

Figure 6.47 A BCD-to-7-segment decoder

Operation	Inputs	Outputs
	s_2 s_1 s_0	F
Clear	0 0 0	0 0 0 0
B − A	0 0 1	$B - A$
A − B	0 1 0	$A - B$
ADD	0 1 1	$A + B$
XOR	1 0 0	$A \text{ XOR } B$
OR	1 0 1	$A \text{ OR } B$
AND	1 1 0	$A \text{ AND } B$
Preset	1 1 1	1 1 1 1

Table 6.1 The functionality of the 74381 ALU

Please see “**portrait orientation**” PowerPoint file for Chapter 6

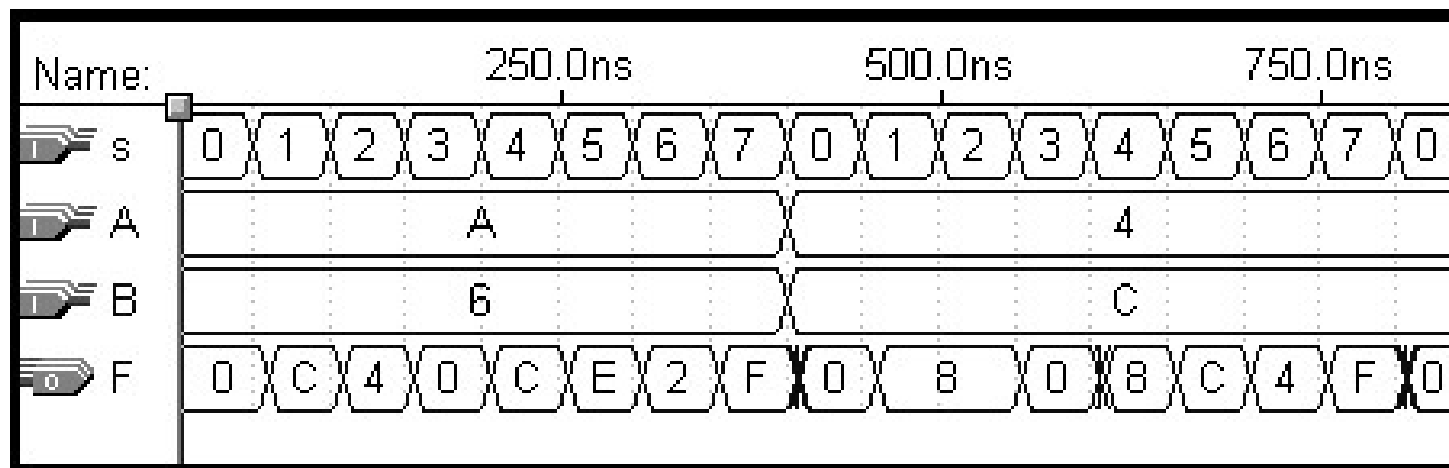


Figure 6.49 Timing simulation for the 74381 ALU code